

Lecture-17


Asynchronous clocked Modulus-12 counter with asynchronous recycling.


On the 12th clock pulse the counter is to be forced to count from '0'. This can be done by dividing 1100.

State sequence:

Clock pulse	Q ₃	Q ₂	Q ₁	Q ₀
Initially	0	0	0	0
1	0	0	0	1
2	0	0	1	0
3	0	0	1	1
4	0	1	0	0
5	0	1	0	1
6	0	1	1	0
7	0	1	1	1
8	1	0	0	0
9	1	0	0	1
10	1	0	1	0
11	1	0	1	1
12(recycles)	0	0	0	0

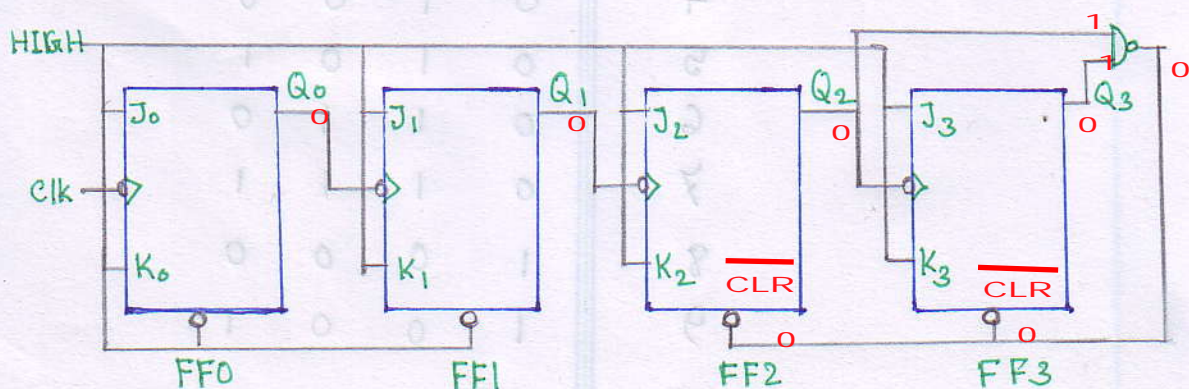A Modulus-12 counter is going to count upto binary value of 0-11. It will recycle at the 12th Clock pulse, and you will only see a slight glimpse of the value 12, after which it will show 0 (that means it will recycle).




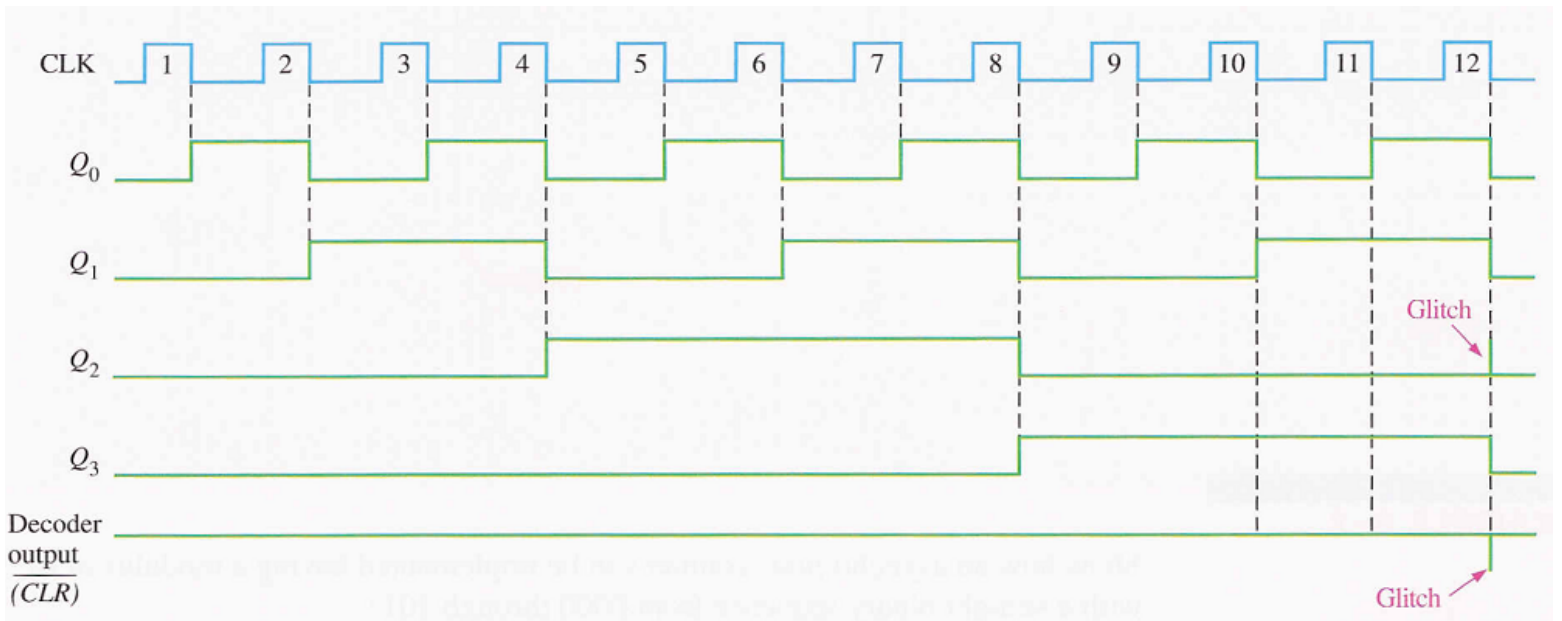


Synchronous Counter:

The Flip-Flops use this synchronous counter are all clocked at the same time by a common clock pulse.

A 2-bit synchronous Binary counter:

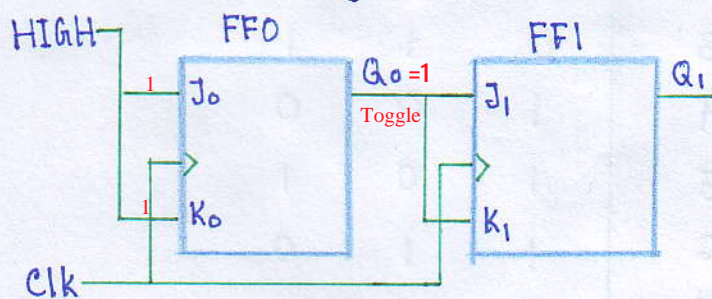

Timing diagram

 

State sequence

Clock pulse	Q ₁	Q ₀
Initially	0	0
1	0	1
2	1	0
3	1	1
4 (recycles)	0	0

Q0 is toggling at every clock cycle

Q1 will only toggle if Q0=1

J0=K0=High

J1=K1=Q0

A 3-bit Synchronous Binary counter

State sequence

Clock pulse	Q_2	Q_1	Q_0
Initially	0	0	0
1	0	0	1
2	0	1	0
3	0	1	1
4	1	0	0
5	1	0	1
6	1	1	0
7	1	1	1
8 (recycles)	0	0	0

Q_0 is toggling at every clock pulse

Q_1 is toggling when and only $Q_0=1$

Q_2 is only toggling if Q_1 and Q_0 both = 1

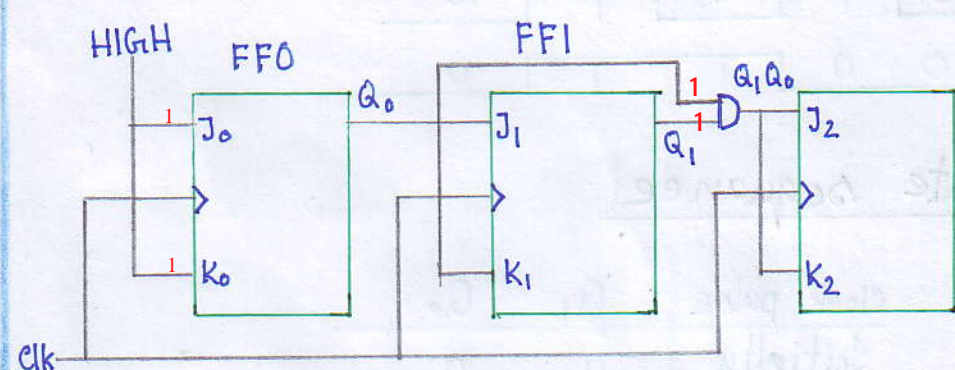


Fig: 3-bit synchronous binary counter

$$J_1 = K_1 = Q_0$$

$$J_0 = K_0 = \text{High}$$

$$J_2 = K_2 = Q_1 Q_0$$

A 4-bit Synchronous Binary Counter:

State sequence:

Clock Pulse	Q_3	Q_2	Q_1	Q_0
Initially	0	0	0	0
1	0	0	0	1
2	0	0	1	0
3	0	0	1	1
4	0	1	0	0
5	0	1	0	1
6	0	1	1	0
7	0	1	1	1
8	1	0	0	0
9	1	0	0	1
10	1	0	1	0
11	1	0	1	1
12	1	1	0	0
13	1	1	0	1
14	1	1	1	0
15	1	1	1	1
16 (recycles)	0	0	0	0

Q_0 is toggling at every clock pulse
So $J_0 = K_0 = 1/\text{High}$

Q_1 is toggling when $Q_0 = 1$
So $J_1 = K_1 = Q_0$

Q_2 is toggling when $Q_1 = 0$ AND $Q_0 = 0$
So $J_2 = K_2 = Q_1 \cdot Q_0$

Q_3 is toggling when $Q_2 = 1$ AND $Q_1 = 1$
AND $Q_0 = 1$
So $J_3 = K_3 = Q_2 \cdot Q_1 \cdot Q_0$

$$J_1 = K_1 = Q_0$$

$$J_0 = K_0 = 1/\text{High}$$

$$J_2 = K_2 = Q_1 \cdot Q_0$$

$$J_3 = K_3 = Q_2 \cdot Q_1 \cdot Q_0$$

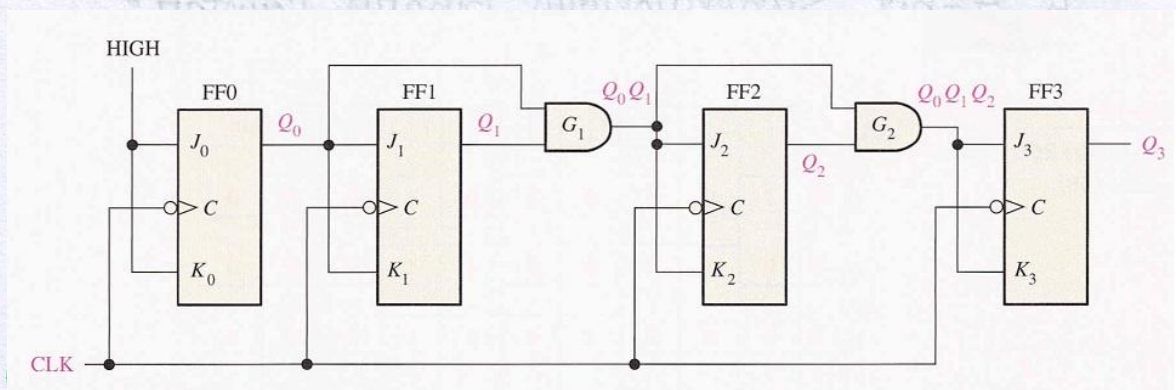


Fig: Synchronous 4-bit Binary counter

Synchronous Decode counter:

State sequence:

Clock Pulse	Q_3	Q_2	Q_1	Q_0
Initially	0	0	0	0
1	0	0	0	1
2	0	0	1	0
3	0	0	1	1
4	0	1	0	0
5	0	1	0	1
6	0	1	1	0
7	0	1	1	1
8	1	0	0	0
9	1	0	0	1
10 (recycles)	0	0	0	0

$$J_1 = K_1 = Q_0 \bar{Q}_3$$

$$J_2 = K_2 = Q_1 Q_0$$

$$J_3 = K_3 = Q_2 Q_1 Q_0 + Q_3 Q_0$$

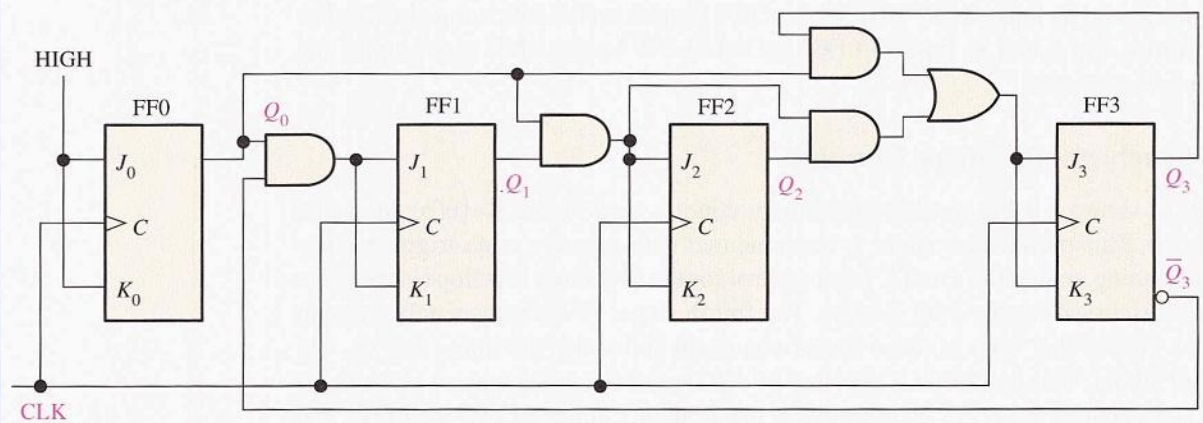


Fig: A Synchronous BCD decode counter

Modulus-12 Synchronous counter
State sequence:

Clock Pulse	Q_3	Q_2	Q_1	Q_0
Initially	0	0	0	0
1	0	0	0	1
2	0	0	1	0
3	0	0	1	1
4	0	1	0	0
5	0	1	0	1
6	0	1	1	0
7	0	1	1	1
8	1	0	0	0
9	1	0	0	1
10	1	0	1	0
11	1	0	1	1
12	0	0	0	0

$$J_0 = K_0 = 1$$

$$J_1 = K_1 = Q_0$$

$$J_2 = K_2 = \bar{Q}_3 Q_1 Q_0$$

$$J_3 = K_3 = Q_2 Q_1 Q_0 + Q_3 Q_1 Q_0$$