

Sub : \_\_\_\_\_

Day

Time :

Date :

# Digital Logic And Circuit

## Midterm Assignment

Course Faculty: Tawsif Ibne Alam

Section: G

Submission Date: 03-07-2021

Name: Nafinur Reo

Id : 20-42195-1

1. a) logic: output of an inverter is opposite of its input.

logic expression:  $x = \bar{A}$ ;  $x = A'$

logic symbol:  $A \rightarrowtail x$

truth table:

A	X
0	1
1	0

b) logic: The output of an OR gate is high whenever one or more input are high, else, of input states, the output is low.

logic expression:  $x = A + B$

logic symbol:  x

truth table:

A	B	C	X
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

c) logic: The output of an AND gate is high when all inputs are high. Else, input is low.

logic expression:  $x = A, B$

logic symbol:  x


Sub:

Name: Nasirunnisa  
Id: 20-12196-1Page \_\_\_\_\_  
Date: / /

truth table:

A	B	C	X
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1


d) logic: The output of an NAND gate is low when all inputs are high. Else, output is high

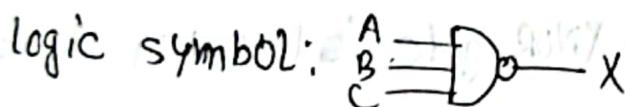logic expression:  $X = \overline{A \cdot B}$ 

truth table:

A	B	C	X
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

e) logic: The output of an NOR gate is low when one or more inputs are high. Else, the output is high.

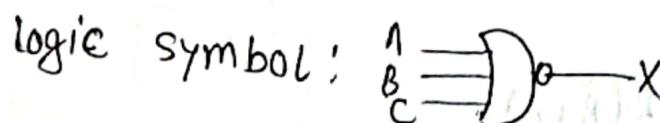logic expression:  $X = \overline{A+B}$ 

truth table:

A	B	C	X
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

Name: Nafisurul Eo  
Id: 20-12195-1

f) logic: The output for XOR gate is high when odd number of inputs are high. Else, output is low.

logic expression:  $X = A \oplus B$

logic symbol: 

truth table:

A	B	C	X
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

g) logic: The output of XNOR gate is low when odd number of inputs are high. Else, output is high.

logic expression:  $X = \overline{A \oplus B}$

logic symbol: 

truth table:

A	B	C	X
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

2. a)  $A\bar{B} + A(\bar{B}+\bar{C}) + B(\bar{B}+\bar{C})$

$$= A\bar{B} + A\bar{B}\bar{C} + B\bar{B}\bar{C}$$

$$= A\bar{B} + A\bar{B}\bar{C} + 0$$

$$= A\bar{B}$$

Sub:

Name: Nasirunnisa

Id: 20-42195-1

Date

Time:


Date: / /

$$\begin{aligned}
 b) & \overline{AB + AC} + \overline{A}\overline{B}C \\
 &= \overline{AB} \cdot \overline{AC} + \overline{A}\overline{B}C \\
 &= (\overline{A} + \overline{B})(\overline{A} + \overline{C}) + \overline{A}\overline{B}C \\
 &= \overline{A}\overline{A} + \overline{A}\overline{C} + \overline{A}\overline{B} + \overline{A}\overline{C} + \overline{A}\overline{B}C \\
 &= \overline{A} + \overline{A}\overline{C} + \overline{A}\overline{B} + \overline{A}\overline{B}C \\
 &= \overline{A} + \overline{A}\overline{B} + \overline{A}\overline{B}C \\
 &= \overline{A} + \overline{A}\overline{B} \\
 &= \overline{A}
 \end{aligned}$$

3. a) i)  $ABC + A\overline{B}\overline{C} + \overline{A}\overline{C}$


$$= ABC + A\overline{B}\overline{C} + \overline{A} + \overline{C}$$

Using basic logic gate we get,

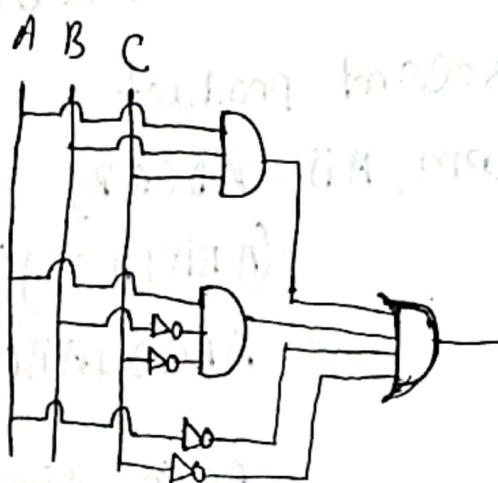

Now, by regarding this

circuits with only NAND gate we get,

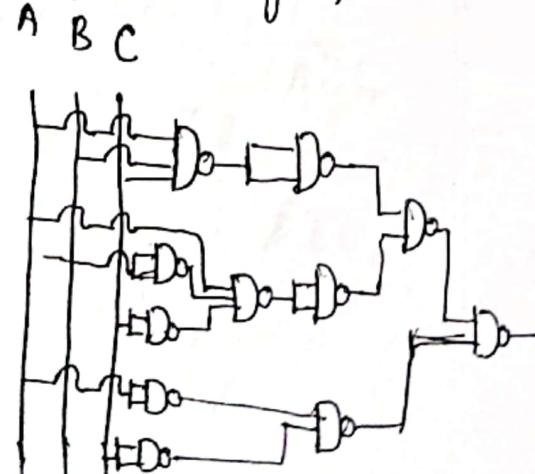


Name: Nasirun Leo  
Id: 20-42396-1

b) i)  $A \bar{B}C + A \bar{B}\bar{C} + \bar{A}C$


$$= A \bar{B}C + A \bar{B}\bar{C} + \bar{A} + \bar{C}$$

Using basic logic gate, we get

A B C

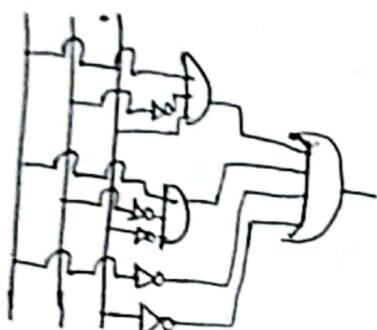

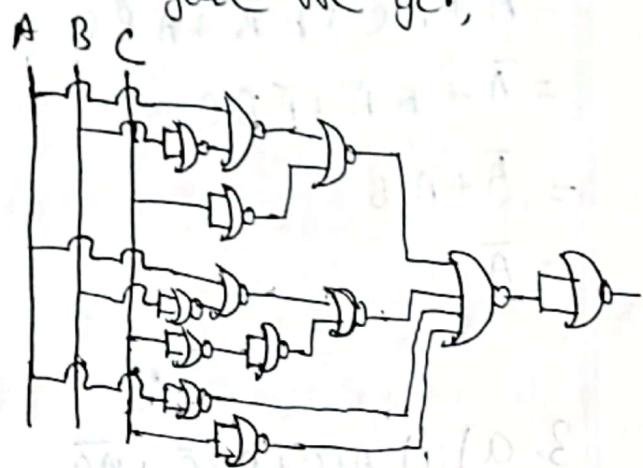Now, by regarding this circuit by using only NOR gate we get,



9. a)  $\bar{A}BC + A\bar{D} + \bar{B}\bar{C}D$

Add input in the first product term,  $\bar{A}BC = \bar{A}BC(D + \bar{D})$   
 $= \bar{A}BCD + \bar{A}BC\bar{D}$

Bringing inputs B and C in the second product :

$$\begin{aligned} \text{term, } A\bar{D} &= A\bar{D}(B + \bar{B}) \\ &= (A\bar{B}\bar{D} + A\bar{B}\bar{D})(C + \bar{C}) \\ &= \bar{A}BC\bar{D} + A\bar{B}C\bar{D} + A\bar{B}\bar{C}\bar{D} \\ &= ABC\bar{D} + A\bar{B}C\bar{D} + A\bar{B}\bar{C}\bar{D} \end{aligned}$$

Sub:

Name / Nafis number

Id: 20-42195-1

Day				
Time				

Bringing input A in the last product term,  $\bar{B}\bar{C}D = \bar{B}\bar{C}D(A + \bar{A})$   
 $= A\bar{B}\bar{C}D + \bar{A}\bar{B}\bar{C}D$

Now, Standard SOP expression =  $\bar{A}BCD + \bar{A}B\bar{C}\bar{D} + A\bar{B}C\bar{D} + A\bar{B}\bar{C}\bar{D}$   
 $+ A\bar{B}\bar{C}\bar{D} + A\bar{B}\bar{C}D + \bar{A}\bar{B}\bar{C}D$

Ex. 5. a)  $A + B(AC + (B + \bar{C})D)$

Bringing input C, D in the first term  $A + B = (A + B) + C\bar{C}$

$$= (A + B + C)(A + B + \bar{C})$$

Now for  $(A + B + C)$ ,

and for  $(A + B + \bar{C})$

$$(A + B + C) + D\bar{D}$$

$$(A + B + \bar{C}) + D\bar{D}$$

$$= (A + B + C + D)(A + B + C + \bar{D})$$

$$= (A + B + \bar{C} + D)$$

$$(A + B + \bar{C} + \bar{D})$$

Bringing missing input in the second term,  $AC + (B + \bar{C}) + D$

$$= (AC + BD + \bar{C}D)$$

Here,  $AC = AC + B\bar{B} = A\bar{B}C + A\bar{B}C$

for  $A\bar{B}C$

for  $A\bar{B}C$

$$= ABC + D\bar{D}$$

$$= A\bar{B}C + D\bar{D}$$

$$= ABCD + A\bar{B}CD$$

$$= A\bar{B}CD + A\bar{B}C\bar{D}$$

Here,  $BD = BD + A\cdot\bar{A} = ABD + \bar{A}BD$

for  $ABD$

for  $\bar{A}BD$

$$= ABD + Q\bar{C}$$

$$= \bar{A}BD + C\bar{C}$$

$$= ABCD + A\bar{B}CD$$

$$= \bar{A}BD + \bar{A}B\bar{C}D$$

Name: Nasirunnisa

Id: 20-12339A-1

$$\text{Here, } CD = \bar{C}D + A \cdot \bar{A}$$
$$= A\bar{C}D + \bar{A}\bar{C}D$$

$$\text{for, } A\bar{C}D$$

$$= A\bar{C}D + B\bar{B}$$

$$= AB\bar{C}D + ABCD$$

$$\text{for, } \bar{A}\bar{C}D$$

$$= \bar{A}\bar{C}D + B\bar{B}$$

$$= A\bar{B}\bar{C}D + \bar{A}BC\bar{D}$$

i. Standard POS expression:  $(A+B+C+D)(A+B+C+\bar{D})(A+B+\bar{C}+D)$

$$(A+B+\bar{C}+\bar{D})(ABC\bar{D} + ABC\bar{D} + ABCD + A\bar{B}CD + ABC\bar{D} +$$

$$A\bar{B}\bar{C}D + \bar{A}BCD + \bar{A}BED + AB\bar{C}D + A\bar{B}\bar{C}D + A\bar{B}CD +$$
$$\bar{A}BCD)$$

$$= (A+B+C+D)(A+B+C+\bar{D})(A+B+\bar{C}+D)(A+B+\bar{C}+\bar{D})$$

$$(\bar{A}BCD + A\bar{B}CD + A\bar{B}CD + A\bar{B}CD + A\bar{B}CD + A\bar{B}CD +$$

$$\bar{A}BCD + A\bar{B}CD + \bar{A}BCD)$$

6. a)  $\bar{A}B + ABC + \bar{AC} + ABC$

$$\text{Now, } \bar{A}B = \bar{A}B(C+\bar{C}) = \bar{A}BC + \bar{A}B\bar{C}$$

$$\bar{AC} = \bar{A} + \bar{C}$$

$$\text{for, } \bar{A} = \bar{A}(B+\bar{B}) = (\bar{A}B + \bar{A}\bar{B})(C+\bar{C}) = \bar{A}BC + \bar{A}B\bar{C} + \bar{A}\bar{B}C +$$

$$\text{for, } \bar{C} = C(A+\bar{A}) = (A\bar{C} + \bar{A}C)(B+\bar{B})$$

$$= ABC + A\bar{B}C + \bar{A}BC + \bar{A}\bar{B}C$$

$$\bar{A}B\bar{C}$$

Name: Nafinun Iro  
Id: 20-13336-1

Standard SOP form:  $\bar{A}BC + \bar{A}\bar{B}C + A\bar{B}C + ABC + A\bar{B}\bar{C} + A\bar{B}C + ABC + A\bar{B}\bar{C} + A\bar{B}C + A\bar{B}C + A\bar{B}\bar{C} + A\bar{B}C + A\bar{B}C + A\bar{B}\bar{C}$

Here, if we use High I/O system, we can develop a truth table. It is SOP form.

$$\therefore Y = \bar{A}BC + \bar{A}\bar{B}C + A\bar{B}C + ABC + A\bar{B}\bar{C} + A\bar{B}C + A\bar{B}\bar{C} + A\bar{B}C + A\bar{B}C + A\bar{B}\bar{C} + A\bar{B}C + A\bar{B}C + A\bar{B}\bar{C}$$
$$= 0 \cdot 1 \cdot 1 + 0 \cdot 1 \cdot 0 + 1 \cdot 1 \cdot 0 + 0 \cdot 0 \cdot 1 + 0 \cdot 0 \cdot 0 + 1 \cdot 0 \cdot 0 + 1 \cdot 0 \cdot 1$$

Truth table:

A	B	C	Y
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

SOP

POS ( $\bar{A}\bar{B}\bar{C}$ )

$$7. a) AC(\bar{B}+C) = ABC + ACC = ABC + AC$$

Convert SOP. for  $AC = AC(B+B) = ABC + A\bar{B}C$

Hence,  $ABC + A\bar{B}C + A\bar{B}C = A\bar{B}C + ABC$

$$= 1 \cdot 0 \cdot 1 + 1 \cdot 1 \cdot 1$$

Name: Mahesh Reddy

ID: 20-12345-1


a) SOP expression:  $AC$

logic gate diagram:



POS expression:  $C(A\bar{C})$

logic gate diagram:

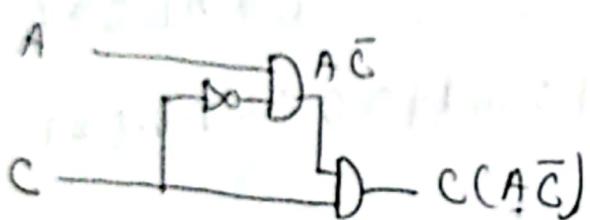

$AB$	$C$	0	1	
00	0	0	1	$\rightarrow$ POS 1-3 $= AC$
01	0	2	0	
11	0	6	1	$\rightarrow$ POS 7-5 $= AC$
10	0	4	1	$\rightarrow$ POS 0-2-6-4 $= C$

b)  $A+BC+CD$

Convert SOP, for  $A = A(B+\bar{B}) = (AB+A\bar{B})(C+\bar{C})$

$$= (ABC + AB\bar{C} + A\bar{B}C + A\bar{B}\bar{C})(D + \bar{D})$$

$$= ABCD + ABC\bar{D} + A\bar{B}\bar{C}D + A\bar{B}\bar{C}\bar{D} + A\bar{B}CD + A\bar{B}\bar{C}D + A\bar{B}C\bar{D}$$

for,  $BC = B\bar{C}(A+\bar{A}) = (AB\bar{C} + \bar{A}B\bar{C})(D + \bar{D})$

$$= AB\bar{C}D + A\bar{B}\bar{C}D + \bar{A}B\bar{C}D + A\bar{B}\bar{C}\bar{D}$$

for,  $CD = CD(A+\bar{A}) = (ACD + \bar{A}CD)(B + \bar{B})$

$$= ABCD + A\bar{B}CD + \bar{A}B\bar{C}D + \bar{A}\bar{B}CD$$

Name: Nasirunnisa

ID: 20-B12325-1


∴ Standard SOP form =  $ABC\bar{D} + ABC\bar{D} + ABC\bar{D} + ABC\bar{D} + ABC\bar{D} + ABC\bar{D}$   
 $\bar{A}\bar{B}C\bar{D} + A\bar{B}\bar{C}D + A\bar{B}\bar{C}\bar{D} + A\bar{B}\bar{C}\bar{D} + A\bar{B}\bar{C}\bar{D} + A\bar{B}\bar{C}\bar{D}$

$Y = ABCD + ABC\bar{D} + ABC\bar{D} + ABC\bar{D} + ABC\bar{D} + ABC\bar{D} + ABC\bar{D}$   
 $+ ABC\bar{D} + \bar{A}BCD + A\bar{B}\bar{C}D + A\bar{B}\bar{C}\bar{D}$

$Y = 1 \cdot 1 \cdot 1 \cdot 1 + 1 \cdot 1 \cdot 1 \cdot 0 + 1 \cdot 1 \cdot 0 \cdot 1 + 1 \cdot 1 \cdot 0 \cdot 0 + 1 \cdot 0 \cdot 1 \cdot 1 + 1 \cdot 0 \cdot 1 \cdot 0$   
 $+ 1 \cdot 0 \cdot 0 \cdot 1 + 1 \cdot 0 \cdot 0 \cdot 0 + 0 \cdot 1 \cdot 0 \cdot 1 + 0 \cdot 1 \cdot 0 \cdot 0 + 0 \cdot 1 \cdot 1 \cdot 1 + 0 \cdot 0 \cdot 1 \cdot 1$


SOP expression:  $\bar{A}CD + A\bar{B}\bar{C} + \bar{A}B\bar{C}\bar{D}$

Logic gate diagram:

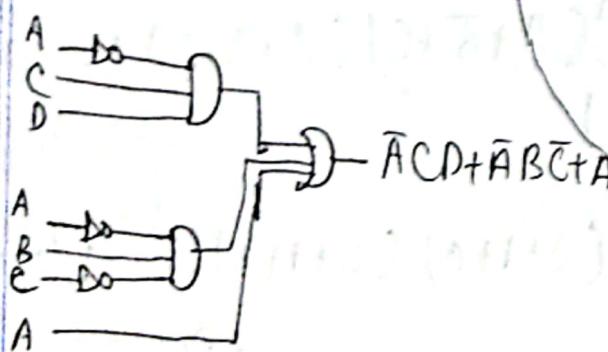

POS expression:  $(A+B+C)(A+\bar{C}+\bar{D})$

Logic gate diagram:

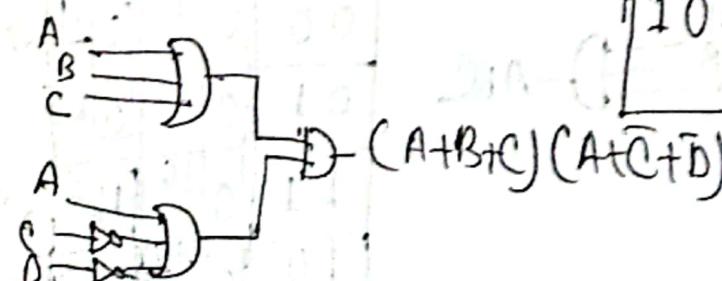

CD	AB	00	01	11	10
00	0	0	1	1	0
01	1	1	1	0	0
11		12	13	15	14
10	1	1	1	1	1
		8	9	11	10

SOP 4-5

$$= \bar{A}B\bar{C}$$

Name: Nishnum Leo  
Id: 2042196-1

Sub:

$$C) A(B+C)(A+C)(A+B+C)(\bar{A}+\bar{B}+\bar{C})$$

Convert POS.

$$\text{For } A = A + (B \cdot \bar{B}) + (A+B)(A+\bar{B})$$

$$\text{Now, } (A+B) + C + \bar{C} = (A + \bar{B}) + C \cdot \bar{C}$$

$$= (A+B+C)(A+\bar{B}+\bar{C}) = (\bar{A}+\bar{B}+C)(A+\bar{B}+\bar{C})$$

$$\text{For, } B+\bar{C} = (B+C) + A \cdot \bar{A} = (A+B+C)(A+\bar{B}+\bar{C})$$

$$\text{For, } \bar{A}+C = (\bar{A}+C) + B \cdot \bar{B} = (\bar{A}+\bar{B}+C)(\bar{A}+\bar{B}+\bar{C})$$


$$Y = (A+B+C)(A+\bar{B}+\bar{C})(A+\bar{B}+C)(A+\bar{B}+\bar{C})(A+\bar{B}+\bar{C})(\bar{A}+\bar{B}+\bar{C}) \\ (\bar{A}+\bar{B}+C)(\bar{A}+\bar{B}+C)$$

$$= (A+B+C)(A+\bar{B}+\bar{C})(A+\bar{B}+C)(A+\bar{B}+\bar{C})(A+\bar{B}+\bar{C}) \\ (\bar{A}+\bar{B}+C)(\bar{A}+\bar{B}+C)$$

$$O = (0+0+0)(0+0+1)(0+1+0)(0+1+1)(1+0+1)(1+0+0)(1+1+0)$$


POS expression:

$$(A+C)(\bar{A}+B)(C)$$

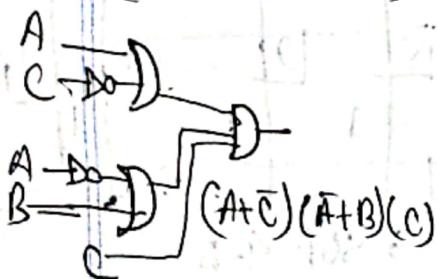

SOP expression:

$$ABC$$

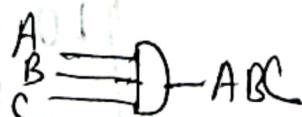

		C		0		1		Pos 0-2-6-4 = C	
		A	B	0	1	0	1	0	1
		0	0	0	0	1	1	Pos 1-3 = A+C	
		0	1	0	2	0	3		
		1	1	0	6	1	7	SOP 7 = ABC	
		1	0	0	4	0	5	Pos 4-5 = A+B	

8xk-map for the given truth table:

AB \ CD		00	01	11	10	
AB	00	1	0	1	1	2
	01	X	1	0	1	6
AB	11	1	X	1	1	19
	10	1	X	1	0	10

④ SOP 0-8      SOP 12-8      SOP 15-11      SOP 6      SOP 15  
 $= \bar{B} \bar{C} \bar{D}$        $= A \bar{C} \bar{D}$        $= ACD$        $= \bar{A} B \bar{C} \bar{D}$        $= \bar{A} B \bar{C} D$

SOP expression:-  $\bar{B} \bar{C} \bar{D} + A \bar{C} \bar{D} + ACD + \bar{A} B \bar{C} \bar{D} + \bar{A} B \bar{C} D$

POS 1      POS 7      POS 14  
 $= A + B + C + \bar{D}$        $= A + \bar{B} + \bar{C} + \bar{D}$        $= A + \bar{B} + C + D$

POS expression:-  $(A + B + C + \bar{D})(A + \bar{B} + \bar{C} + \bar{D})(\bar{A} + \bar{B} + \bar{C} + D)$

b) using don't care values:-

$$SOP \ 0-4-2-6$$

$$= \bar{A} \bar{D}$$

$$SOP \ 0-4-12-8$$

$$= \bar{C} \bar{D}$$

$$SOP \ 8-9-11-10$$

$$= A \bar{B}$$

$$SOP \ 5-13$$

$$= B \bar{C} D$$

$$SOP \ 13-15-9-11$$

$$= A D$$

		CD	00	01	11	10
		AB	00	01	11	10
00	00	1	0	X	X	2
00	01	X	1	5	7	6
01	11	12	X	13	15	14
01	10	8	9	11	13	16
10	11	1	X	1	X	
10	10	1	X	1	X	

$$\therefore SOP \ expression = A \bar{D} + \bar{C} \bar{D} + A \bar{B} + B \bar{C} D + A D$$

$$POS(1-3) \quad POS \ 3-7$$

$$= A B + \bar{D}$$

$$= A + \bar{C} + \bar{B}$$

$$= \bar{A} + \bar{B} + \bar{C} + D$$

$$POS \ expression = (A B + \bar{D}) (A + \bar{C} + \bar{B}) (\bar{A} + \bar{B} + \bar{C} + D)$$

c) After solving, using don't care and not using don't care, I think using don't care value is more useful. Because don't care values helps us increasing the size of the group. So, I can easily simplified the pos as well as sop expression.

Here is my solution, while not using don't care I got 5 sop expression and 3 pos expression. Beside while using don't care I got the same but the grouping size was bigger than it.

Sub

$$9. 1) F(A, B, C, D) = \underline{\underline{z}}(3, 7, 8, 12, 15)$$

$$Q(A, B, C, D) = (1, 5, 9, 10, 11)$$

$\therefore$  S.O.P. expression

$$= \bar{A}CD + BCD + A\bar{C}\bar{D}$$

2) SOP expression:

$$= CD + A\bar{B} + A\bar{C}\bar{D}$$

$$\text{POS expression} = (A+C)(\bar{C}+B)(C+\bar{B})$$

$$= A \bar{B}$$

3) After solving using don't care and not using don't care, we see 1 thing using don't care value is more useful. Because don't care value helps us increasing the size of the group so I can easily simplified the pos as well as sop expression.

Here in my solution, while not using don't care I got 3 SOP expression. Beside, while using don't care, I got the same but the grouping size was bigger than not using don't care grouping.


AB	CD	00	01	11	10	
00	0,	X	1	1	0	SOP 3-7 = ACD
01	0	X	5	7	0	
11	3	12	13	15	14	SOP 7-15 = BCD
10	0	8	9	11	10	SOP 2-6-14-10 = C+D
						SOP 12-8 = A C D
						SOP 8-9-11-10 = C+D

Name: Nafisunnesa  
Id: 20-92395-1

10. a) truth table: sum(S) and carry(Cout) of a


Half Adder.

Now, by using basic gate:

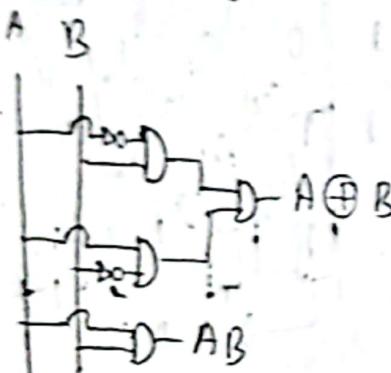

A	B	S	Cout
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

Now, by using NAND gate:

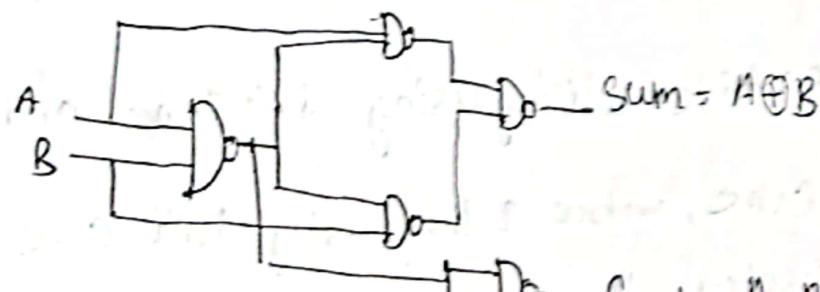


Total 5 NAND gates are required to implement half adder.


11.B) truth table: Difference(D) and Borrow(B) of a half subtractor:

A	B	D	B
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

Now, by using basic gate:

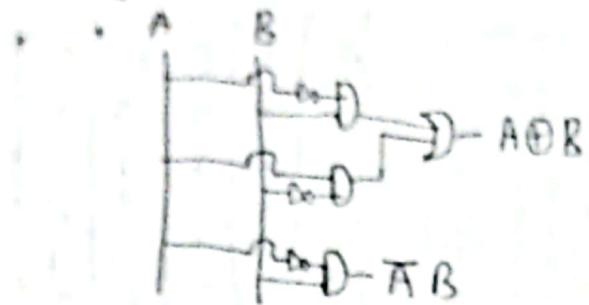


Now, by using NOR gate:

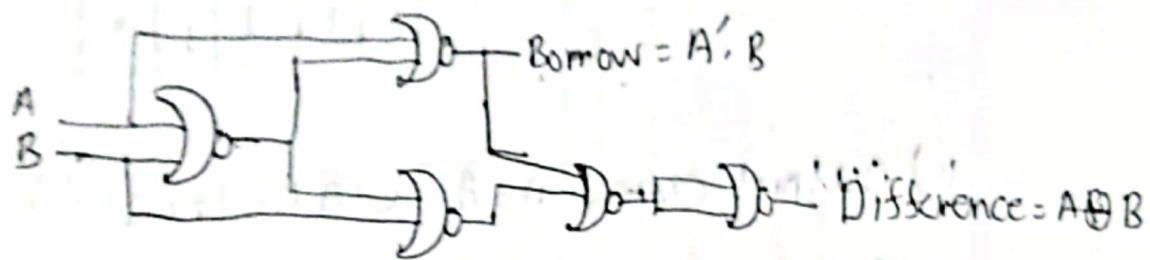


total 5 NOR gate are required to implement half subtractor.

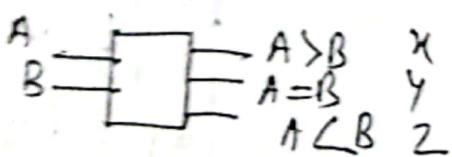12. For 1-bit magnitude comparator, there will be 2 input, 3 output.



A	B	A > B	A = B	A < B
0	0	0	1	0
0	1	0	0	1
1	0	1	0	0
1	1	0	1	0

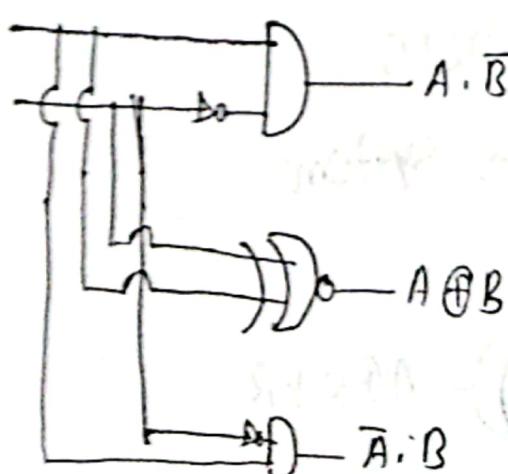

$$X = A \cdot B̄$$

$$Y = A \cdot B + Ā \cdot B̄$$

$$Z = Ā \cdot B$$

SOP expression =  $A \cdot B̄ + (A \oplus B) + Ā \cdot B$

Sub:

Name: Nabinur Leo  
Id: 20-42196-1

13. i) truth table of the system:

A	B	C	$\alpha$	y
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	1
1	1	1	1	1

ii) Output expression =  $\bar{A} \bar{B} C + \bar{A} B \bar{C} + A \bar{B} \bar{C} + A B C + \bar{A} B C + A B \bar{C}$ 

$$\begin{aligned} & \text{SOP 2-3-6-7} \quad \text{SOP 6-4} \quad \text{SOP 1-3} \\ & = B \bar{A} C \quad = A \bar{C} \quad = \bar{A} C \end{aligned}$$

Minimized output expression

$$\begin{aligned} &= A \bar{C} + \bar{A} C + B \\ &= A \oplus C + B \end{aligned}$$

A	B	C	0	1	2	3	4	5
0	0	0	0	1	1	1	1	1
0	1	1	1	1	0	0	0	0
1	1	1	1	0	1	1	0	0
0	10	1	1	0	1	0	1	0

iii) Output expression =  $A \oplus C + B$ 

logic diagram for the system:



Sub:

Name: Nasirun Leo  
Id : 20-4019h-J

Date:

Time:

Data:

14. truth table of the system:

A	B	C	D	Z
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
1	0	0	0	0
1	0	0	1	0
1	0	1	0	1
1	0	1	1	1
1	1	0	0	0
1	1	0	1	0
1	1	1	0	1
1	1	1	1	1

ii)  $Z = \overline{A}BCD + \overline{A}BC\bar{D} + \overline{A}B\bar{C}D + A\overline{B}CD + A\overline{B}\bar{C}D + ABC\bar{D} + ABCD$

SOP 7-6-15-14    SOP 15-14-11-10    SOP 3-7-15-11

$$= BC$$


$$= AC$$

$$= CD$$

∴ minimized output expression =  $BC + AC + CD$

iii) Output expression =  $BC + AC + CD$

logic diagram for the system

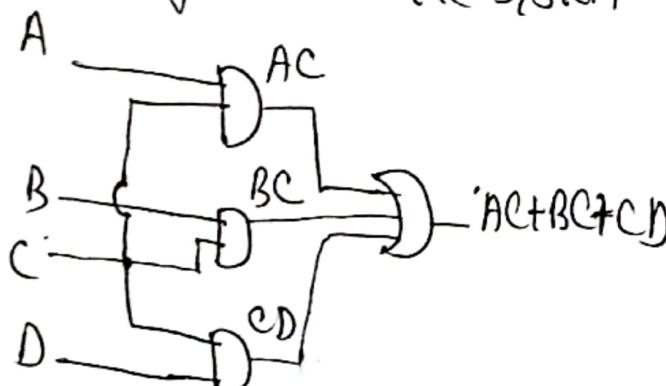

AB	00	01	11	10
00	0	0	1	1
01	0	1	0	0
11	0	1	0	1
10	0	0	1	0