

Lecture - 15

The Edge-Triggered J-K Flip-Flop:

The functioning of the J-K Flip-flop is identical to that of the S-R flip-flop in the SET, RESET and NO change conditions of operation. The different is that the J-K flip-flop has no invalid states as does the S-R Flip-Flop.


 


Fig: Logic diagram for a positive edge triggered J-K Flip-Flop.


Inputs			Output		Comments
J	K	clk	Q	\bar{Q}	
0	0	↑	Q_0	\bar{Q}_0	No change
0	1	↑	0	1	RESET
1	0	↑	1	0	SET
1	1	↑	\bar{Q}_0	Q_0	Toggle

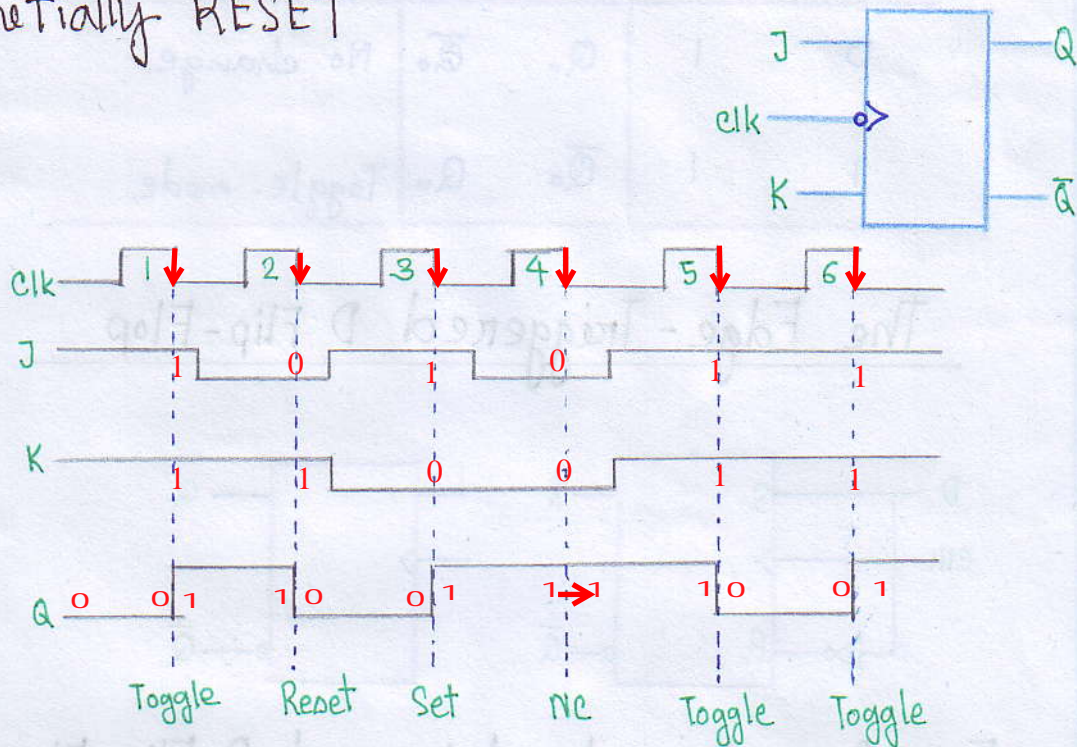Determine Q output if the J-K Flip-Flop is initially RESET



T Flip-Flop:

 A J-k flip-flop commented for toggle operation is sometimes called a T Flip-Flop.



Inputs		Outputs		Comments
T	clk	Q	\bar{Q}	
0	1	Q_0	\bar{Q}_0	No change
1	1	\bar{Q}_0	Q_0	Toggle mode

The Edge-Triggered D Flip-Flop

 


Fig: A positive edge-triggered D Flip-Flop Formed with an S-R Flip-Flop and an inverter.


Truth table for positive edge-triggered D Flip-Flop:

Inputs		Outputs		Comments
D	clk	Q	\bar{Q}	
1	↑	1	0	Set
0	↑	0	1	Reset

The D Flip-Flop is used to store a single data bit position edge-triggered Flip-Flop stores data at the leading edge of the clock.

negative edge triggered

 Determine Q if the \uparrow D Flip-Flop is initially ReSet



S-R Flip-flop inputs (S & R)


J-K Flip flop inputs (J & K)

T Flip-flop input (T)

D Flip-Flop input (D)

(S & R, J & K, T, D) all of these inputs are known as synchronous inputs

Flip-Flop with Asynchronous Inputs

 


$\overline{\text{PRE}}$ and $\overline{\text{CLR}}$ are known as asynchronous inputs for flip-flops. They are active low in nature.

$\overline{\text{PRE}}$ =PRESET=SET Operation, Q=1

$\overline{\text{CLR}}$ =CLEAR= RESET Operation Q=0


Fig: Logic symbol for a J-K Flip-Flop with active Low preset & clear inputs.

* Determine Q for the following inputs.

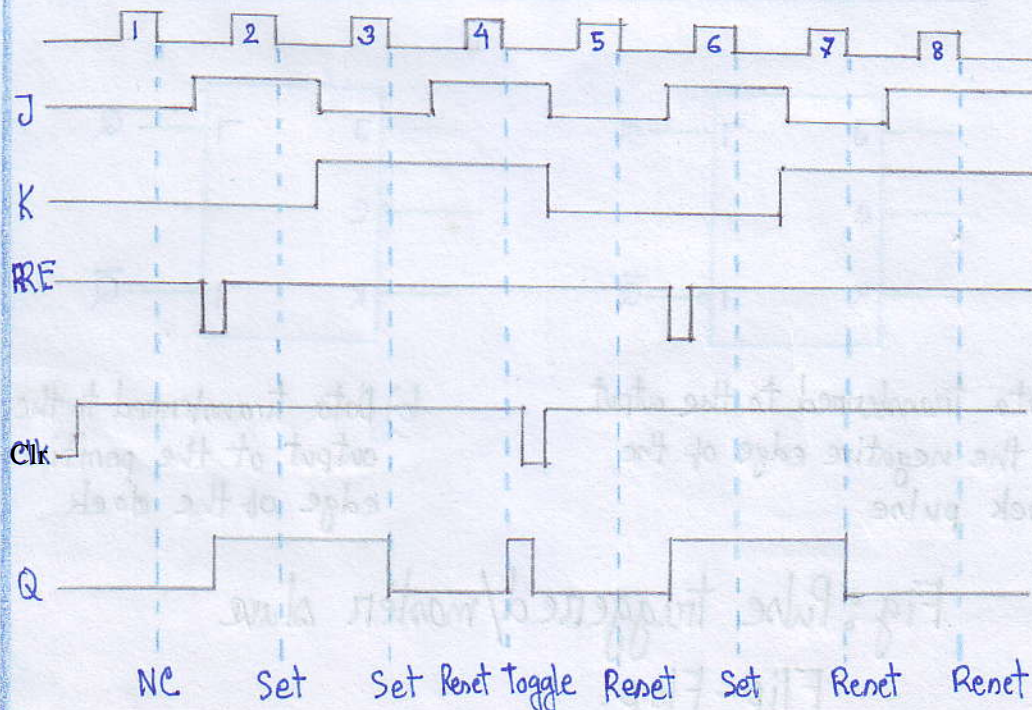

negative edge triggered

 Determine Q if the \uparrow D Flip-Flop is initially ReSet



S-R Flip-flop inputs (S & R)


J-K Flip flop inputs (J & K)

T Flip-flop input (T)

D Flip-Flop input (D)

(S & R, J & K, T, D) all of these inputs are known as synchronous inputs

Flip-Flop with Asynchronous Inputs

 


$\overline{\text{PRE}}$ and $\overline{\text{CLR}}$ are known as asynchronous inputs for flip-flops. They are active low in nature.

$\overline{\text{PRE}}$ =PRESET=SET Operation, $Q=1$

$\overline{\text{CLR}}$ =CLEAR= RESET Operation $Q=0$

Fig: Logic symbol for a J-K Flip-Flop with active

 Determine the output Q for the positive edge triggered J-K flip-flop, if it is initially at reset condition. Here the $\overline{\text{PRE}}$ and $\overline{\text{CLR}}$ are asynchronous active low preset and clear operation respectively.



MASTER SLAVE FLIP-FLOPS


 



Fig: Logic diagram for a master slave J-k Flip-Flop.

Truth table:

Inputs			Outputs		Comments
J	K	clk	Q	\bar{Q}	
0	0	\downarrow	Q_0	\bar{Q}_0	No change
0	1	\downarrow	0	1	Reset
1	0	\downarrow	1	0	Set
1	1	\downarrow	\bar{Q}_0	Q_0	Toggle

 


 a) Data transferred to the output at the negative edge of the clock pulse



b) Data transferred to the output at the positive edge of the clock

Fig: Pulse triggered/master slave Flip-Flop.

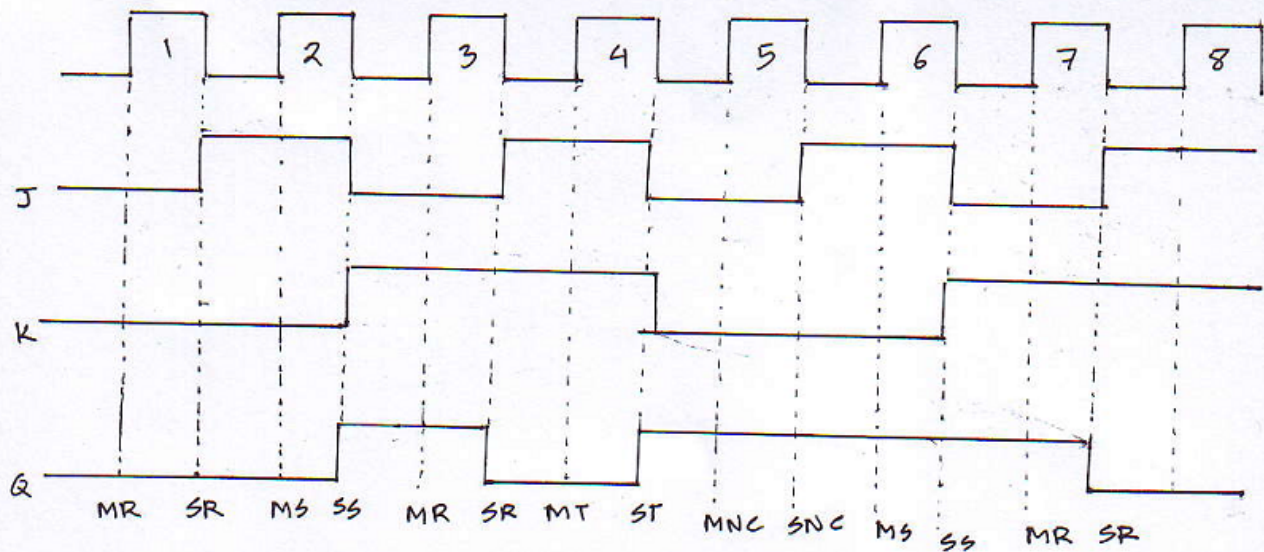

Determine Q if the flip-flop is initially RESET

D type edge triggered Flip-Flop without pulse transition detector.

 


Fig: D type positive edge triggered Flip-Flop
Truth-table of $\bar{S}\bar{R}$ latch

\bar{S}	\bar{R}	Q
0	1	1
1	0	0
0	0	Invalid
1	1	NC

CP	D	\bar{S}	\bar{R}	G1	G
0	0	1	1	0	1
1	0 → 1	1	0	0	1
0	1	1	1	1	0
1	1 → 0	0	1	1	0