

Assignment-Midterm

Digital Logic & Circuits

Basic Logic Gate (2 Points)

1. Write down the truth table, logic, logic expression and draw the logic symbol for each of the following gates with 3 inputs.

a. NOT (1 input)	b. OR	c. AND	d. NAND
e. NOR	f. XOR	g. XNOR	

Logic Simplification with Boolean algebra: (1 Points)

2. Using **Boolean algebra** and **De Morgan's Rule** where applicable, simplify the following expressions

a. $A\bar{B} + A(\bar{B} + \bar{C}) + B(\bar{B} + \bar{C})$

b. $\overline{AB + AC} + \bar{A}\bar{B}C$

Building Combinational Logic Circuit and Universal Gates: (2 Points)

3. For the following output expressions, **design the combinational logic circuits with basic logic gates (use Boolean algebra to reduce the expressions where possible)**.
- a. For the designed logic circuits, **redraw** each of them with only **Universal NAND gates only**.
i. $ABC + A\bar{B}\bar{C} + \bar{A}C$
- b. For the designed logic circuits, **redraw** each of them with only **Universal NOR gates only**.
i. $A\bar{B}C + A\bar{B}\bar{C} + \bar{A}C$

Types of Boolean Expressions (2 Points)

4. **Convert** the following to **Standard SOP expressions**:
a. $\bar{A}BC + A\bar{D} + \bar{B}CD$
5. **Convert** the following to **Standard POS expressions**:
a. $A + B(AC + (B + \bar{C})D)$
6. **Develop a truth table from each of the following expressions. (Hint: Convert them to their standard forms before you create any truth table)**
a. $\bar{A}B + AB\bar{C} + \bar{A}C + A\bar{B}C$

Karnaugh Map (3 Points)

7. **Use K-map** to find the **minimum SOP and POS expression** from the following expressions **and draw the logic gate diagrams**.
- a. $AC(\bar{B} + C)$
- b. $A + B\bar{C} + CD$
- c. $A(B + \bar{C})(\bar{A} + C)(A + \bar{B} + C)(\bar{A} + B + \bar{C})$

Don't Care Condition: (6 Points)

8. The following is a **truth-table** of a **combinational logic circuit**. With **inputs A, B, C, D** and **output F**.

Fill-up a K-MAP out of the truth-table.

A	B	C	D	F
0	0	0	0	1
0	0	0	1	0
0	0	1	0	X
0	0	1	1	X
0	1	0	0	X
0	1	0	1	1
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	X
1	0	1	0	X
1	0	1	1	1
1	1	0	0	1
1	1	0	1	X
1	1	1	0	0
1	1	1	1	1

- Derive the **simplified expression** using **K-map** (without using **don't care values**).
- Derive the **simplified expression** using **K-map** (using **don't care values**).
- Using your results in parts **a** and **b**, **explain the importance** of using **don't care terms**.

9. Consider the given expression:

$$F(A,B,C,D) = \sum (3,7,8,12,15)$$

$$d(A,B,C,D) = (1,5,9,10,11)$$

where **d(A,B,C,D)** represents the **don't care conditions**.

Fill-up a K-MAP with the above data.

- Derive the **simplified SOP expression** using **K-map** (without using **don't care values**).
- Derive the **simplified expression** using **K-map** (using **don't care values**).
- Using your results in parts 1 and 2, **explain the importance** of using **don't care terms**

Adder-Subtractor: (4 Points)

10. Derive the **truth-table** and corresponding **output expressions** of **Sum (S)** and **Carry (C_{out})** of a **Half-Adder** having **inputs A** and **B**. For the derived expression, design the **combinational logic circuit** using **basic logic gates**.

- Use the above logic circuit to redesign the **Half-Adder** using only **NAND gates**.

11. Derive the **truth-table** and corresponding **output expressions** of **Difference (D)** and **Borrow (B)** of a **Half-Subtractor** having **inputs A** and **B**. For the derived expression, design the **combinational logic circuit** using **basic logic gates**.

- Use the above logic circuit to redesign the **Half-Subtractor** using only **NOR gates**.

Magnitude Comparators: (2 Points)

12. Design a **1-bit Magnitude Comparator**. State **how many input and output terminals** your device will have with **proper markings in a block diagram**. For your design show the **truth table**, derive **SOP output expressions** and **draw combinational logic diagram**.

Complex Digital System Design: (8 Points)

13. You are hired to design a system that can be used in a safety push button lock device. There will be three buttons for example **A, B and C**. If **odd number of inputs are** pressed, the lock mechanism opens. In any other case the lock mechanism remains closed. If any of **two buttons** is pressed simultaneously, **an alarm sounds**. Let's say **X** is the lock mechanism and **Y** is the alarm that makes the sound,
- construct a truth-table for the system and
 - find the minimized output expression using Boolean algebra or k-map
 - draw the logic diagram for the system.
14. In a departmental store hired you to design a cash register, operated by four personnel- the store manager (A), the assistant manager (B), the cashier (C) and the chief accountant (D). At least two of these personnel must be present, along with the cashier, for the register to unlock. Design a logic system that can perform this operation. For your design, show the truth-table, write the simplified output expression and a draw logic diagram.
- construct a truth-table for the system and
 - find the minimized output expression using Boolean algebra or k-map
 - draw the logic diagram for the system

Instructions:

- You must complete the assignment, solely by yourself, with ethics and self-belief. Plagiarism, copying from your peers/ or any other source will cause you to loose all the marks.
- Answers must be handwritten, clear to read and properly numbered, and every page must have your name and I.D on top right corner of your page.
- You must use CAMSCANNER tool to take picture, convert it to pdf and then upload. Please do not upload individual pictures. It should be a complete pdf.
- Deadline for submission of Assignment is on 3rd July 2021 (, 2:00 P.M, in MS TEAMS. A a portal has been opened already.
- Failure to follow the instructions mentioned above, will cause you to lose marks.