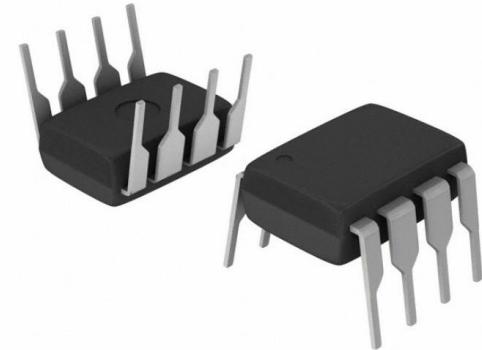


Digital Electronics

555 Timer

What is IC 555?


- The IC 555 timer is a one type of chip used in different applications like an oscillator, pulse generation, timer.
 - The operating range of this IC ranges from 4.5V -15V DC supply.
 - The functional parts of the 555 timer IC include **flip-flop**, **voltage divider** and a **comparator**.
 - The main function of this IC is to generate an accurate timing pulse.
-



Pin configuration of IC 555

- **GND Pin:** Pin-1 is a GND pin which is used to supply a zero voltage to the IC.
- **Trigger Pin:** Pin-2 is a trigger pin which is used to convert the FF from set to reset. The output of the timer depends on the amplitude of the external trigger pulse that is applied to the trigger pin.
- **Output Pin:** Pin-3 is an output pin.
- **Reset Pin:** Pin-4 is a Reset pin. When the negative pulse is applied to this pin to disable or reset, a false triggering can be neglected by connecting to VCC.


DIP chip (Dual-Inline package)

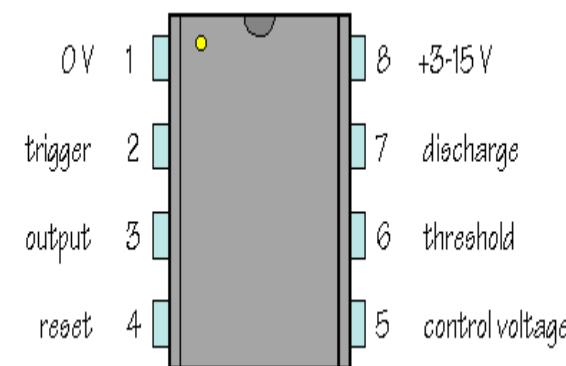

Pin configuration of IC 555 (contd...)

- **Control Voltage Pin:** Pin-5 is the control voltage pin used to control the pulse width of the output waveform and also the levels of threshold and trigger. When an external voltage is applied to this pin, then the output waveform will be modulated
- **Threshold Pin:** Pin-6 is the threshold pin, when the voltage is applied to threshold pin, then it contrasts with a reference voltage. The set state of the FF can be depends on the amplitude of this pin.
- **Discharge Pin:** Pin-7 is the discharge pin, when the output of the open collector discharges a capacitor between the intervals, then it toggles the output from high to low.
- **Supply Terminal:** Pin-8 is the voltage supply pin which is used to supply the voltage to the IC with respect to the ground terminal.

DIP chip (Dual-Inline package)

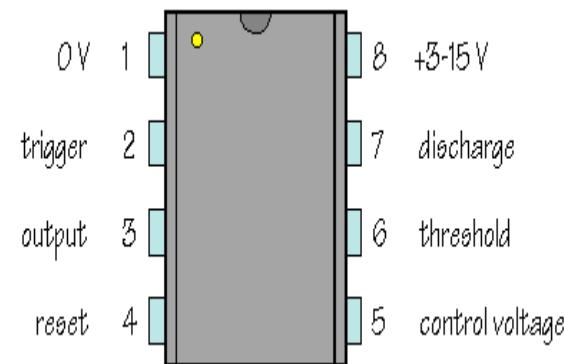

Basic Operation of IC 555

- When the normally HIGH trigger input momentarily goes below $1/3 V_{cc}$, the output of comparator B switches from LOW to HIGH and sets the S-R latch ($Q=1$). causing the output (pin 3) to go HIGH and turning the discharge transistor Q1 off.
- When the LOW threshold input goes above $2/3 V_{cc}$ and causes the output of comparator A to switch from LOW to HIGH. This resets the latch ($Q=0$), causing the output (pin 3) to go back LOW and turning the discharge transistor on.
- Note: The trigger and threshold inputs are controlled by external components connected to produce either monostable or astable action.

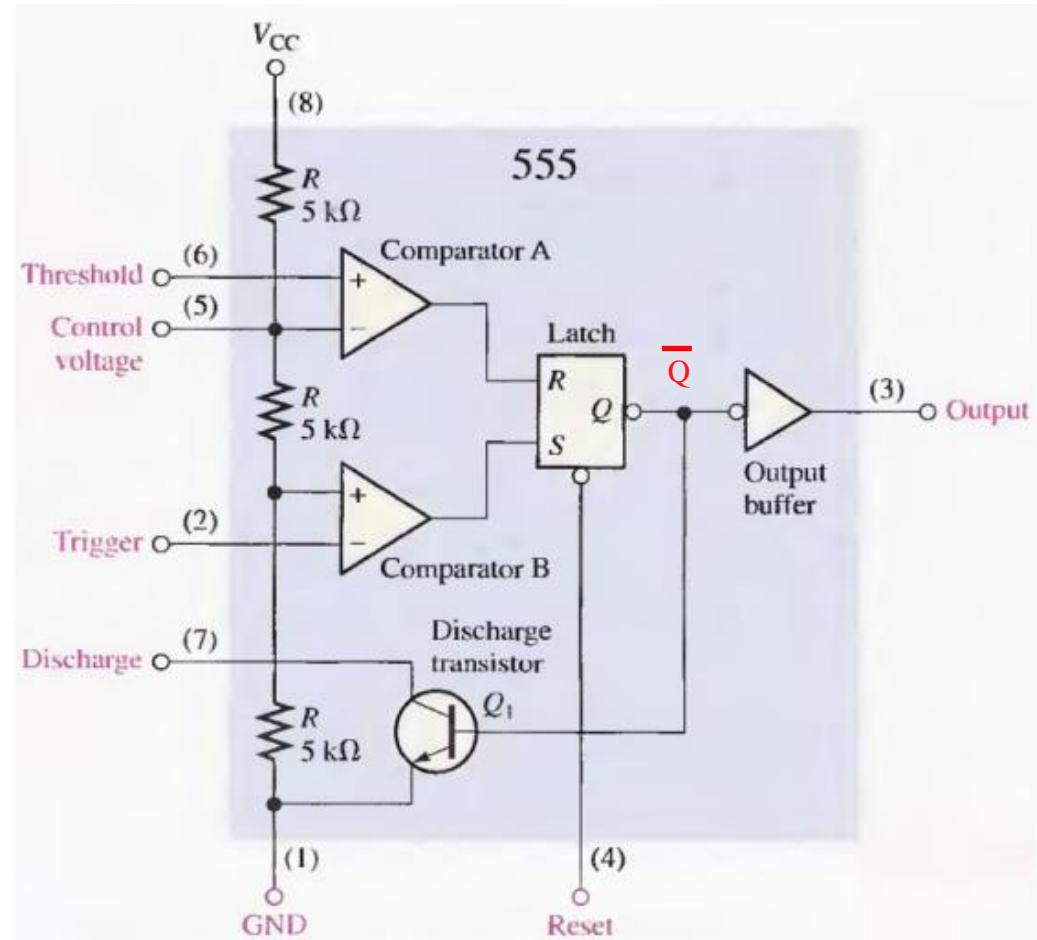


Fig 1. Internal functional diagram of a 555 timer.

Modes of IC 555 timer

- Time Delay Mode

- In the time delay mode, the delay is controlled by one external resistor and capacitor.
- Also Known as **Monostable (One-shot) mode.**

Example: Turn a light ON in a delayed amount of time.
(Just turn ON or OFF once)

- Oscillator Mode

- In the oscillator mode, the frequency of oscillation are controlled with two external resistors and one capacitor.
- Also known as **Astable mode.**

Example: Can make a light flash at a specific rate.
(Can turn ON and OFF repeatedly)




- Another mode is Bistable Mode

IC 555 timer : *Astable Mode*

Astable multivibrator mode schematic

Notice:

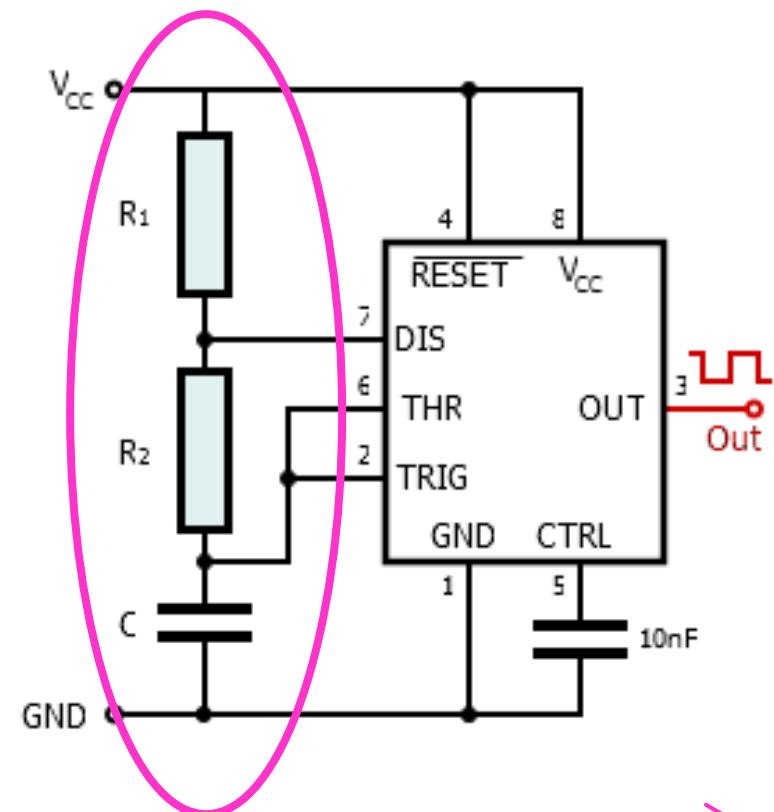- 2 resistors
- 1 capacitor
- OUTPUT is square wave pulses



IC 555 timer : *Astable Mode*

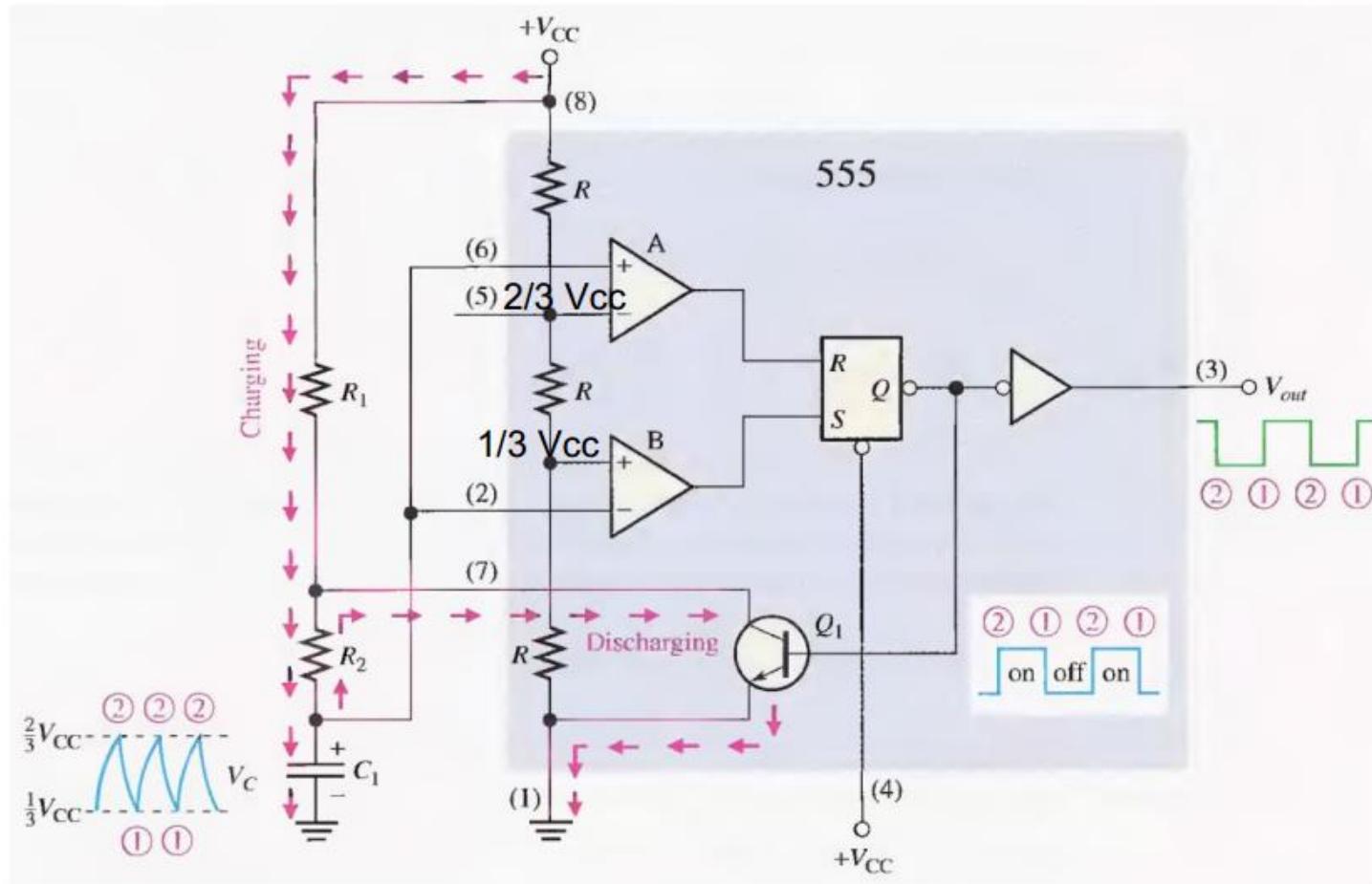


Fig. Operation of the 555 timer in the astable mode.

IC 555 timer : *Astable Mode*

Operation

- Initially, when the power is just turned on, the capacitor (C_1) remain '**Uncharged**' and thus the trigger (pin 2) and threshold (pin 6) is at **0 V**. So, V_{out} (comp. A) = 0 and V_{out} (comp. B) = 1. That's why Q1 is **OFF**.
- Now, **C1** begins **charging** through R_1 and R_2 , indicated in Figure. When, C_1 is just above $2/3V_{cc}$ then V_{out} = (comp A)=1 and V_{out} = (comp B)=0 which Resets the latch ($Q=0$).
- At this state **Q1** turns **ON** and creates a **discharging** path as shown in the figure. When C_1 discharge it causes V_{out} (comp. A)=0 and when C_1 discharges down to $1/3V_{cc}$ then V_{out} (comp. B)=1.
- This again Sets latch and turning off Q1 again. Another charging cycle begins and the entire process repeats.


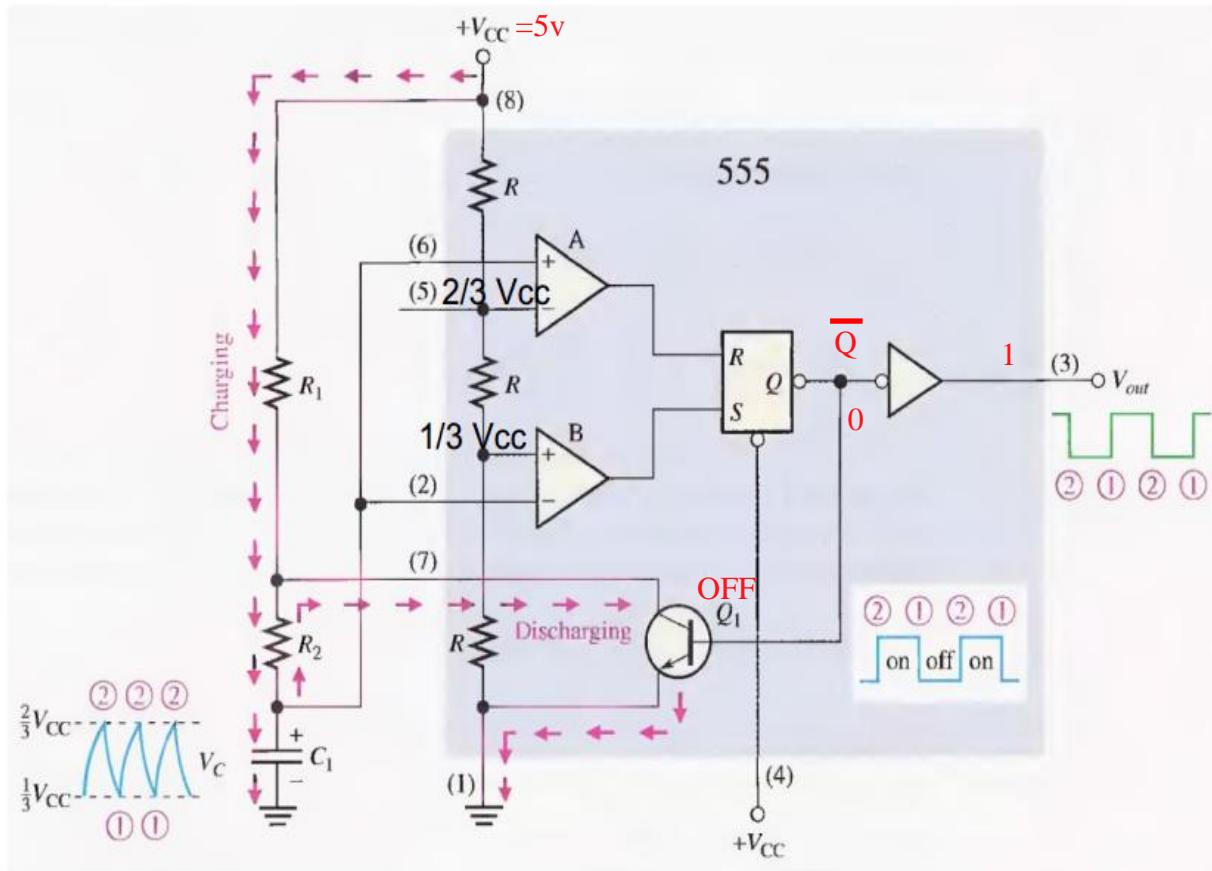
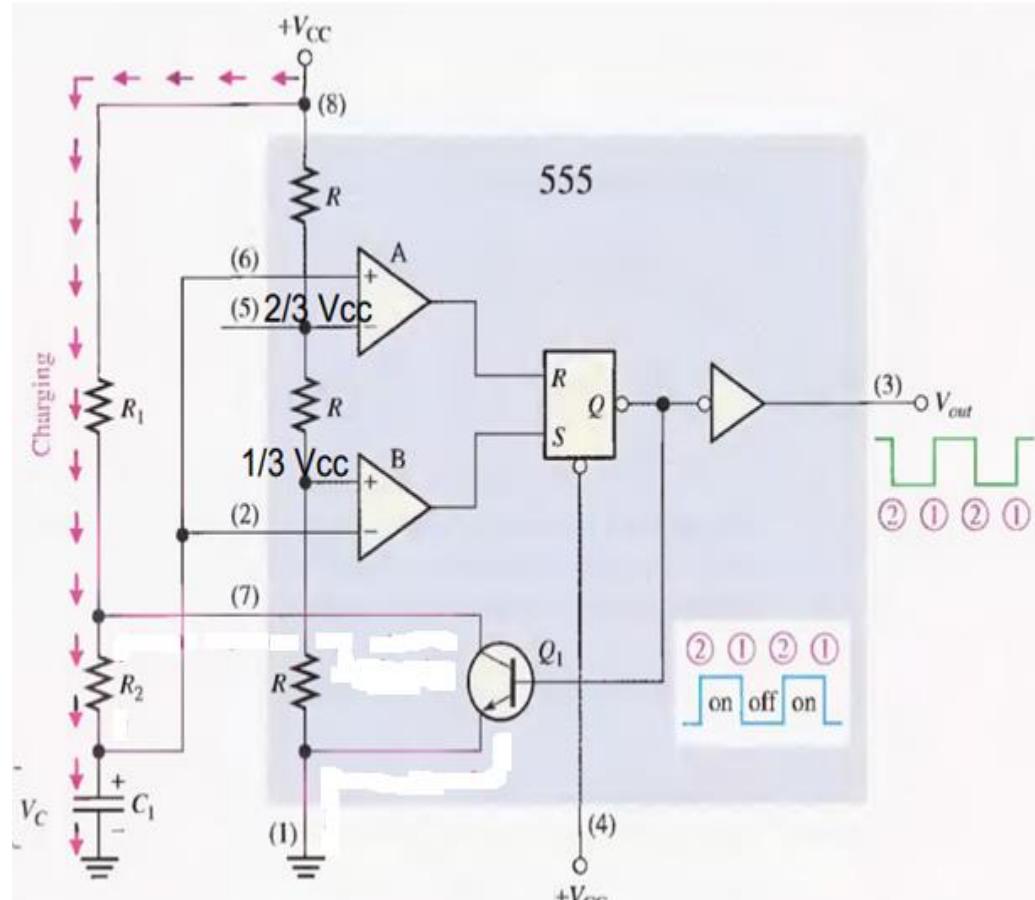


Fig. Operation of the 555 timer in the astable mode.

IC 555 timer : *Astable Mode*

t_{HIGH} : Calculations for the Oscillator's HIGH Time

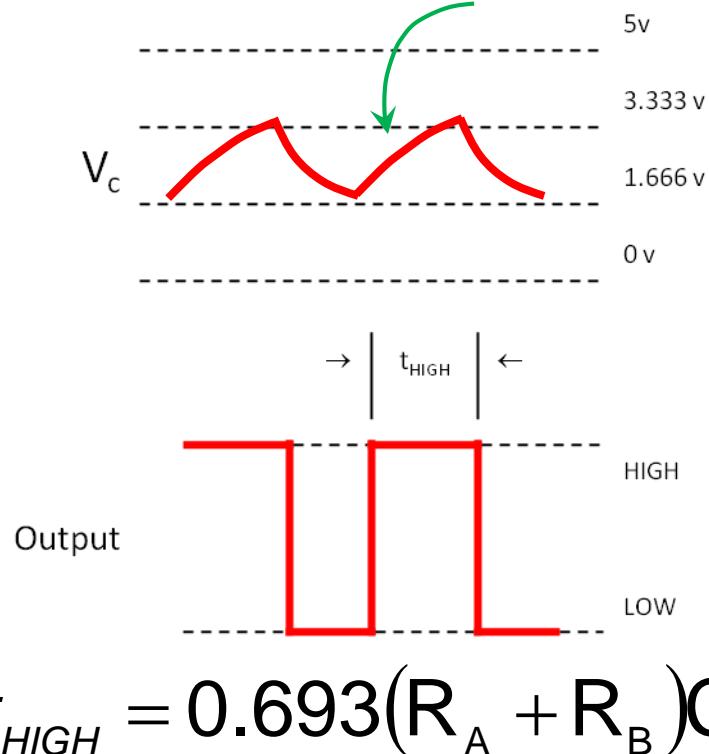
THE OUTPUT IS HIGH WHILE THE CAPACITOR IS
CHARGING THROUGH $R_A + R_B$.




IC 555 timer : *Astable Mode*

t_{LOW} : Calculations for the Oscillator's LOW Time

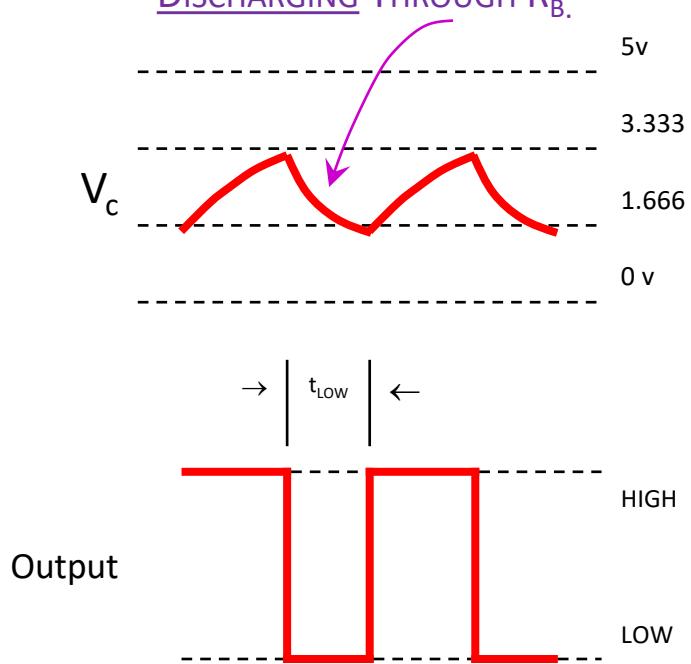THE OUTPUT IS LOW WHILE THE CAPACITOR IS
DISCHARGING THROUGH R_B .



$$t_{\text{LOW}} = 0.693 R_B C$$

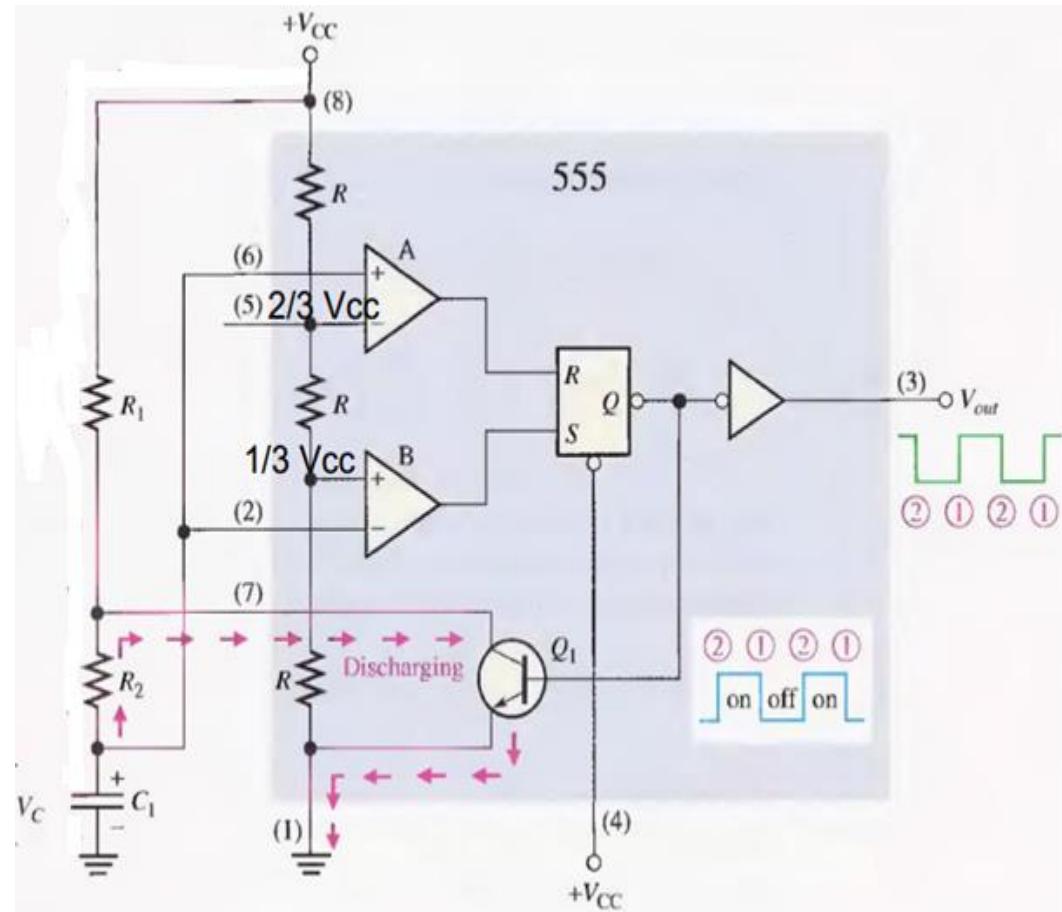

IC 555 timer : *Astable Mode*

Time Period:

The Period is the total time of an on/off cycle and depends on the values of R_A , R_B , and C


$$t_{HIGH} = 0.693(R_A + R_B)C$$

$$t_{LOW} = 0.693R_B C$$

$$T = t_{HIGH} + t_{LOW}$$

$$T = [0.693(R_A + R_B)C] + [0.693R_B C]$$

$$T = 0.693(R_A + 2R_B)C$$

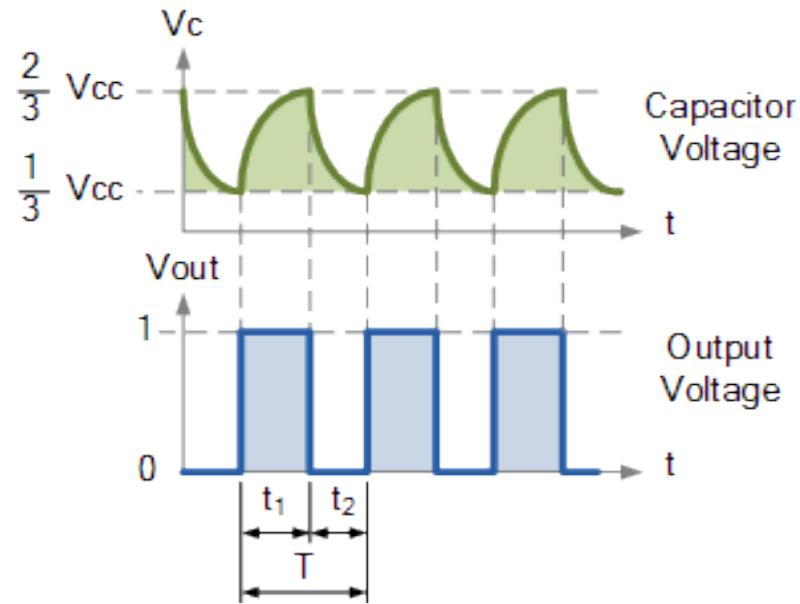

Notes:

- The value 0.693 is a factor associated with the charge/discharge cycle of the 555 timer.


IC 555 timer : *Astable Mode*

Frequency :

The frequency of an oscillation (or anything that exhibits a repeating pattern) is inversely proportional to the period

$$F = \frac{1}{T}$$

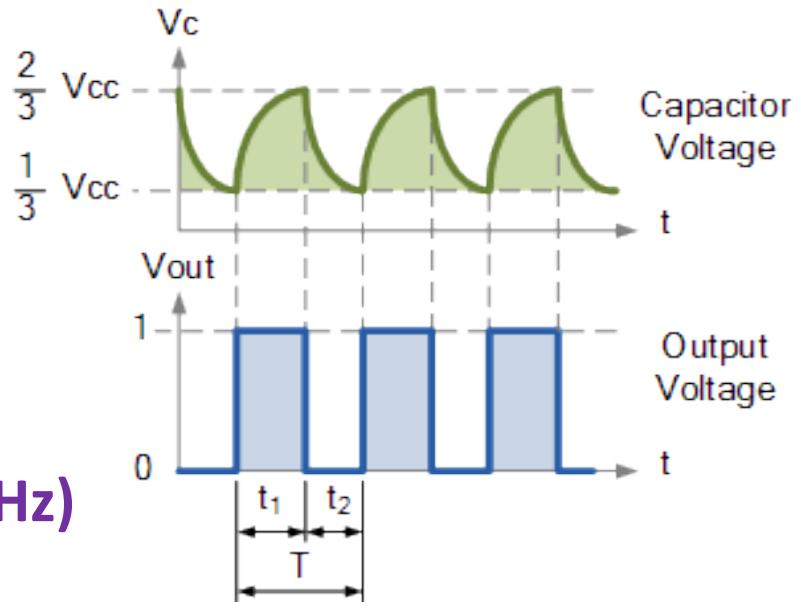
Unit of Measure:
cycles/second = Hertz (**Hz**)



$$F = \frac{1}{0.693 (R_A + 2R_B) C}$$

Mathematical Problem

- Design an oscillator for a frequency of 200Hz with a duty cycle of 78%. Determine time period, high & low time, R_B and R_A (assume $C=10\mu F$)

1. Determine Period (T):

$$T = \frac{1}{F} = \frac{1}{200\text{Hz}} = 0.005\text{s}$$

2. Determine T_H and T_L :

$$T_H = 78\% \bullet 0.005\text{s} = 0.0039\text{s} = 3.9\text{ms}$$

$$T_L = 22\% \bullet 0.005\text{s} = 0.0011\text{s} = 1.1\text{ms}$$

Mathematical Problem (*contd...*)

3. Determine R_B by using the T_L equation:

$$T_L = 0.693R_B C$$

$$1.1\text{ms} = 0.693 \cdot R_B \cdot 10\mu\text{F}$$

$$R_B = 158.7\Omega$$

4. Determine the value of R_A :




$$T_H = 0.693(R_A + R_B)C$$

$$3.9\text{ms} = 0.693(R_A + 158.7\Omega)10\mu\text{F}$$

$$562.8\Omega = R_A + 158.7\Omega$$

$$R_A = 404.1\Omega$$


IC 555 timer : Monostable Mode

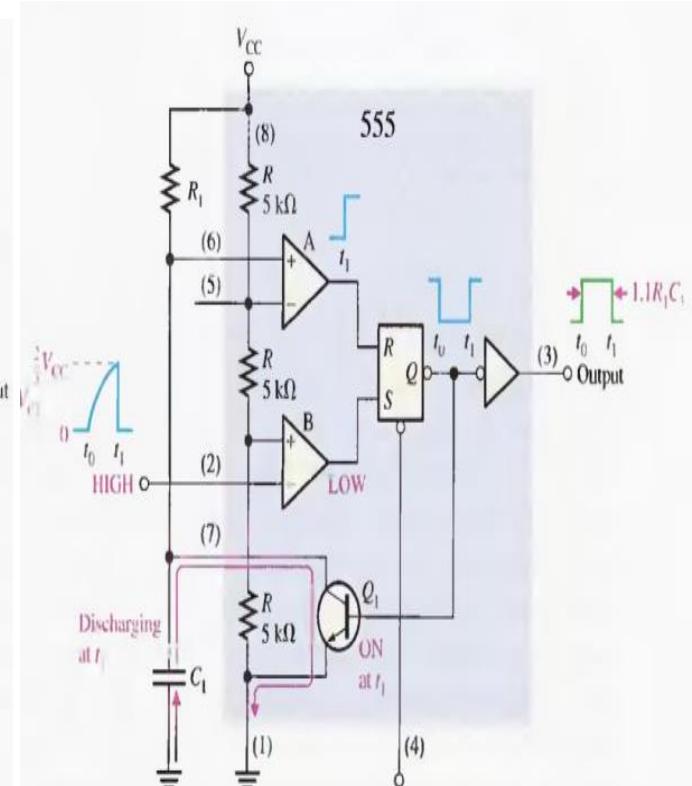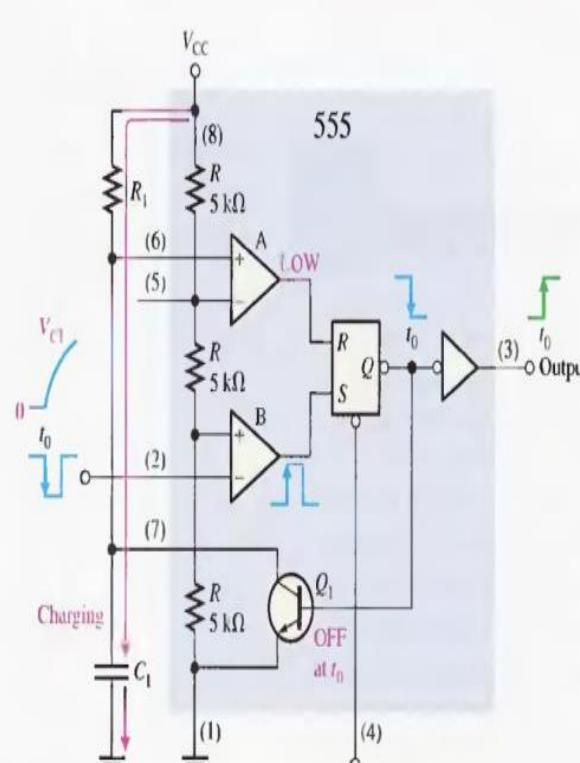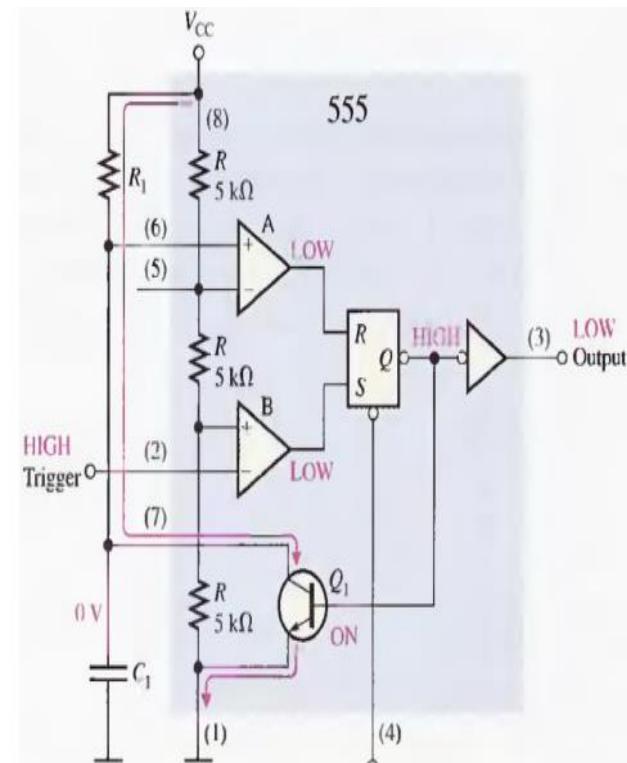

IC 555 timer : Monostable Mode



Before a trigger pulse is applied, the output is LOW (**Stable off-state**) and the discharge transistor Q1 is ON, keeping C1 discharged as shown in Figure.

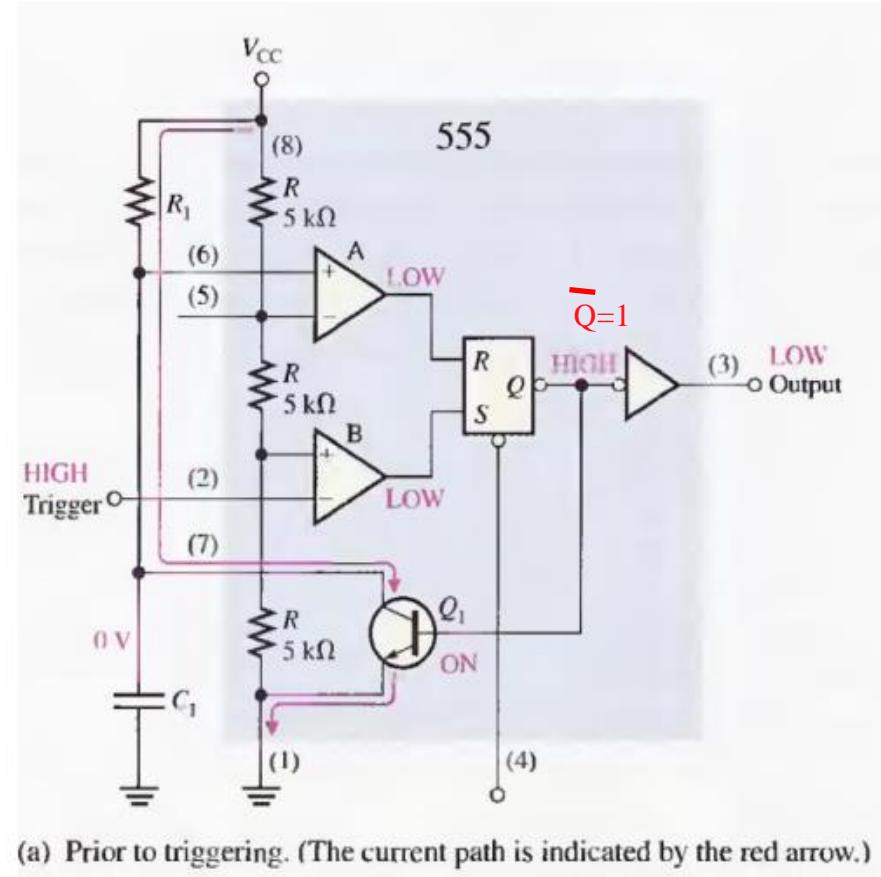Note: Before a trigger pulse, it is equal to Vcc .



IC 555 timer : Monostable Mode

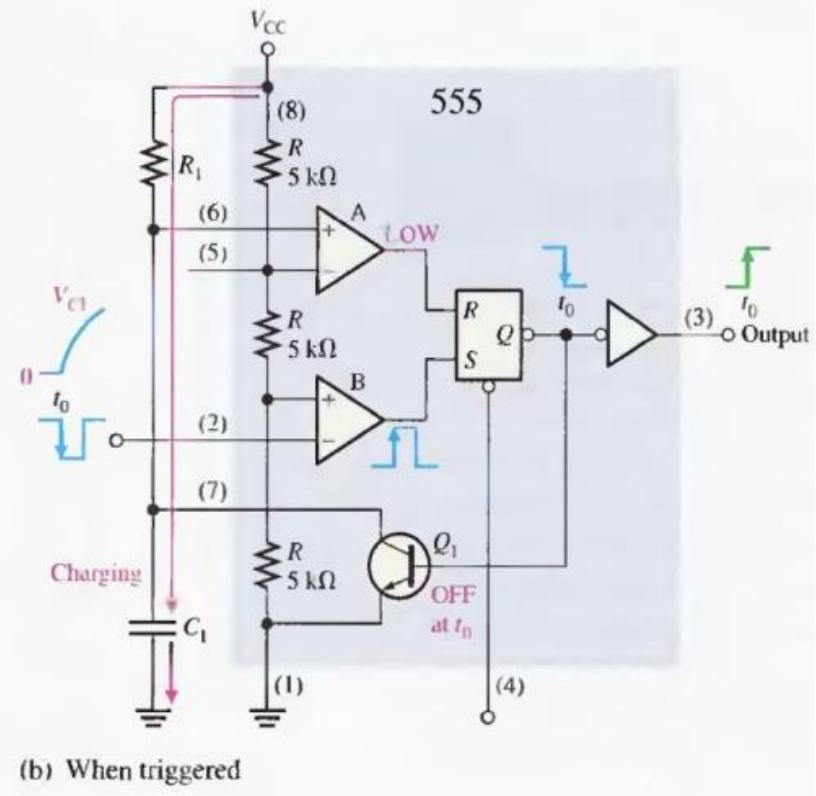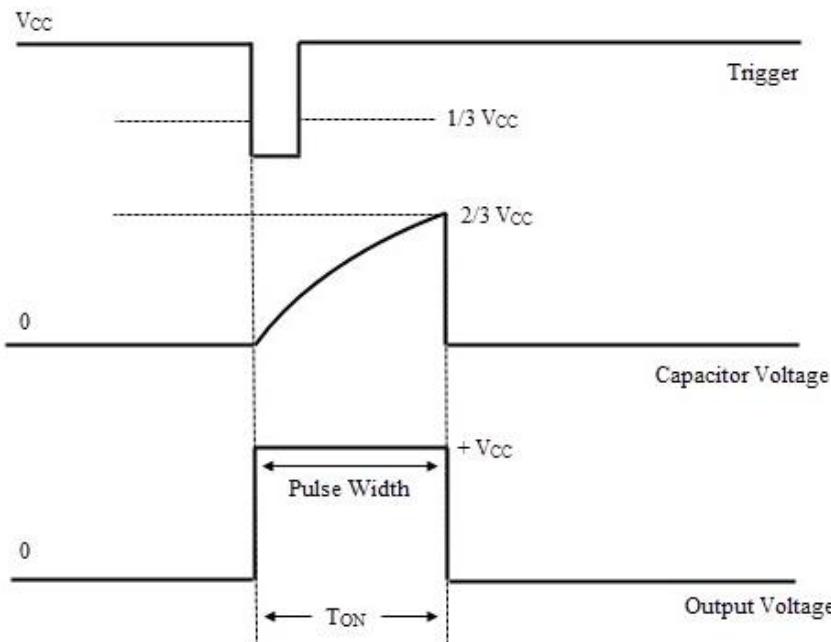At time, t_0 a negative going triggering pulse is applied and it becomes less than $1/3 V_{CC}$; then (+ve) i/p > (-ve) i/p for comp. B.




So, Comp. B = 1 which makes Output = High. Q1 is off and allowing C1 to charge through R1 as shown in Figure.

IC 555 timer : Monostable Mode

At time, t_1 when C_1 is just above $2/3 V_{CC}$ then (+ve) i/p > (-ve) i/p for comp. A. So, Comp. A = 1.

At the same time, (-ve) i/p of comp. B (HIGH) > (+ve) i/p of comp. B ($1/3$ of V_{CC}). So, comp. B = 0.

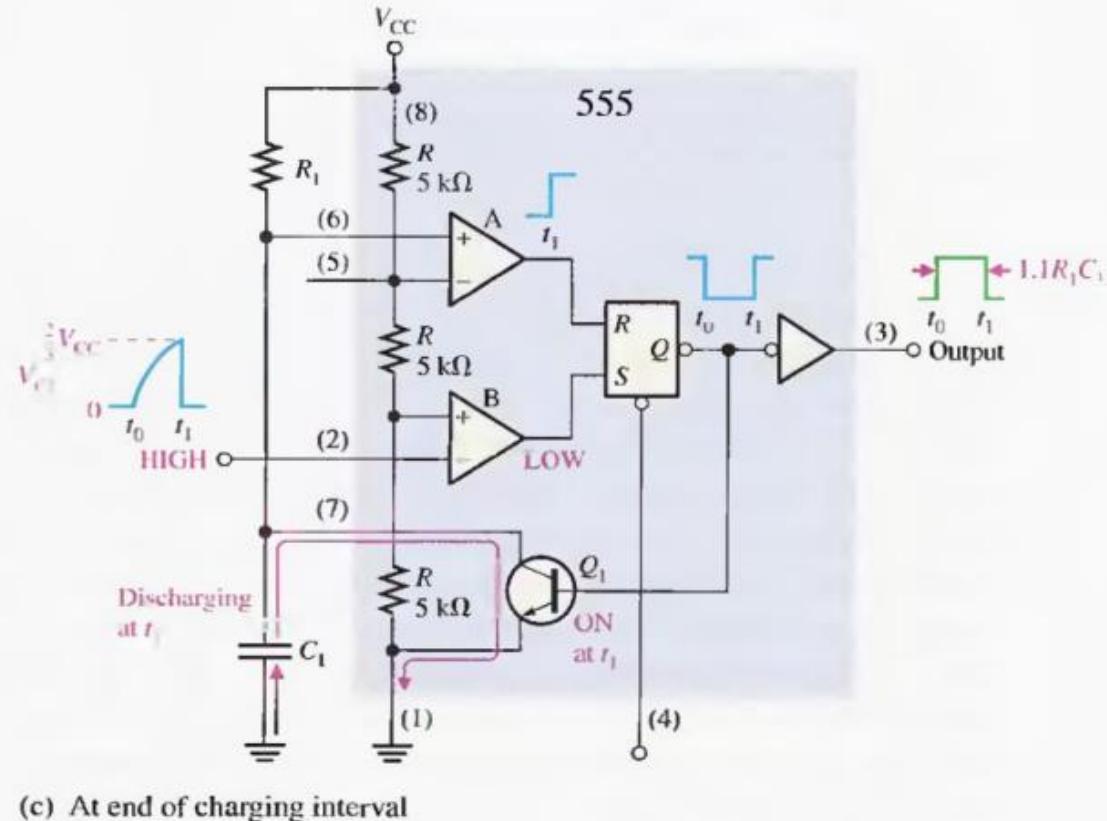Thus o/p = 0 (LOW) at t_1 state. This turns on Q1 and helps C_1 to discharge.



- The pulse width of the output is determined by the time constant of R_1 and C_1 :

$$t_w = 1.1 R_1 C_1$$

Thank You

Figure 7–51 shows three 74LS122 one-shots connected as a sequential timer. This particular circuit produces a sequence of three 1 s pulses. The first one-shot is triggered by a switch closure or a low-frequency pulse input, producing a 1 s output pulse. When the first one-shot (OS 1) times out and the 1 s pulse goes LOW, the second one-shot (OS 2) is triggered, also producing a 1 s output pulse. When this second pulse goes LOW, the third one-shot (OS 3) is triggered and the third 1 s pulse is produced. The output timing is illustrated in the figure. Variations of this basic arrangement can be used to produce a variety of timed outputs.

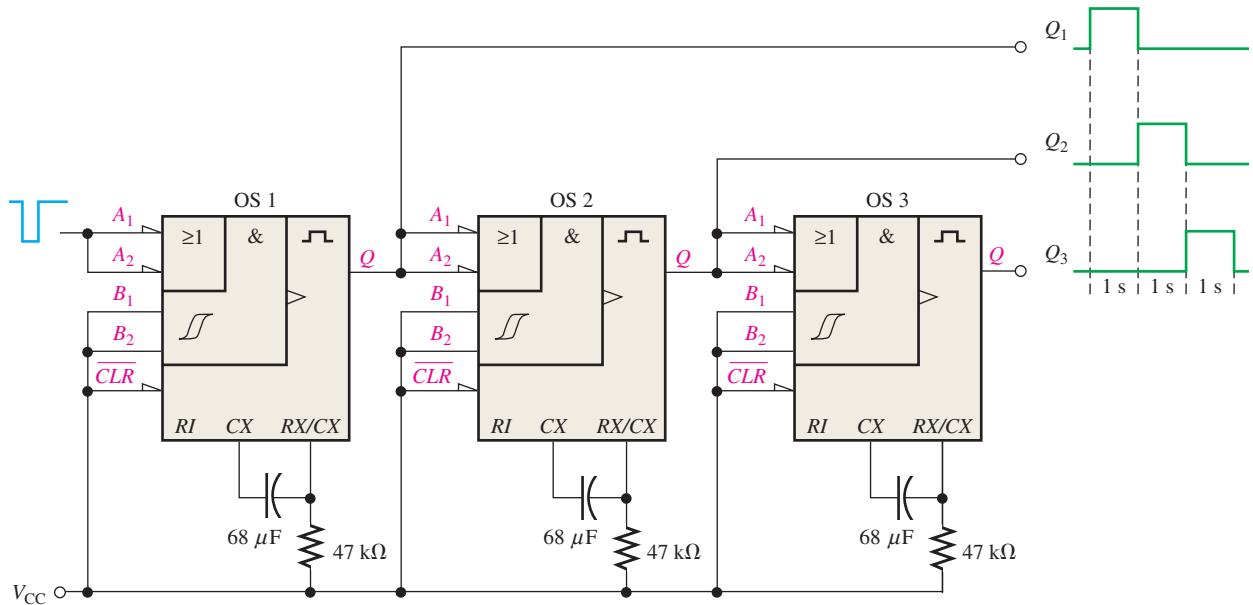


FIGURE 7–51 A sequential timing circuit using three 74LS122 one-shots.

The 555 Timer as a One-Shot

The 555 **timer** is a versatile and widely used IC device because it can be configured in two different modes as either a monostable multivibrator (one-shot) or as an astable multivibrator (pulse oscillator). The astable multivibrator is discussed in Section 7–6.

The 555 Timer Operation

A functional diagram showing the internal components of a 555 timer is shown in Figure 7–52. The comparators are devices whose outputs are HIGH when the voltage on the positive (+) input is greater than the voltage on the negative (−) input and LOW when the − input voltage is greater than the + input voltage. The voltage divider consisting of three $5\text{ k}\Omega$ resistors provides a trigger level of $\frac{1}{3} V_{CC}$ and a threshold level of $\frac{2}{3} V_{CC}$. The control voltage input (pin 5) can be used to externally adjust the trigger and threshold levels to other values if necessary. When the normally HIGH trigger input momentarily goes below $\frac{1}{3} V_{CC}$, the output of comparator B switches from LOW to HIGH and sets the S-R latch, causing the output (pin 3) to go HIGH and turning the discharge transistor Q_1 off. The output will stay HIGH until the normally LOW threshold input goes above $\frac{2}{3} V_{CC}$ and causes the output of comparator A to switch from LOW to HIGH. This resets the latch, causing the output to go back LOW and turning the discharge transistor on. The external reset input can be used to reset the latch independent of the threshold circuit. The trigger and threshold inputs (pins 2 and 6) are controlled by external components connected to produce either monostable or astable action.

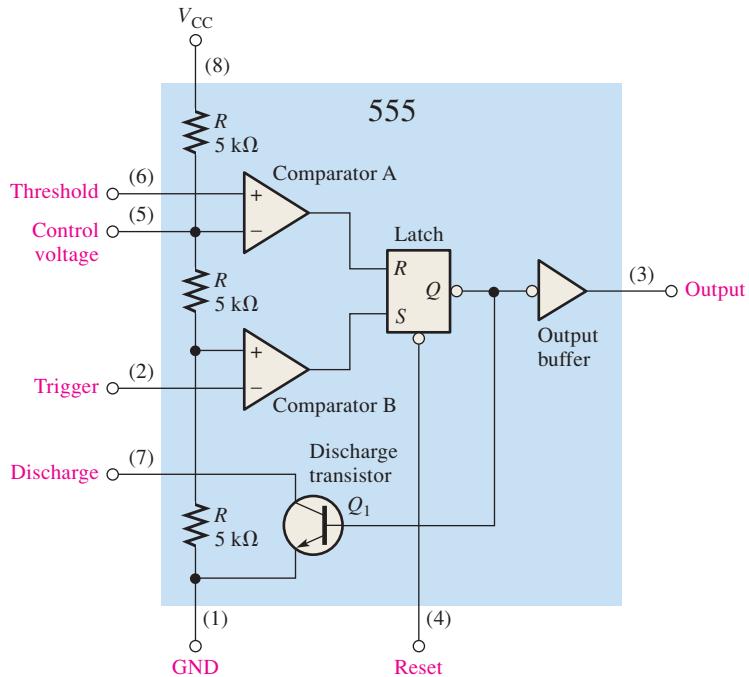


FIGURE 7–52 Internal functional diagram of a 555 timer (pin numbers are in parentheses).

Monostable (One-Shot) Operation

An external resistor and capacitor connected as shown in Figure 7–53 are used to set up the 555 timer as a nonretriggerable one-shot. The pulse width of the output is determined by the time constant of R_1 and C_1 according to the following formula:

$$t_W = 1.1R_1C_1 \quad \text{Equation 7–3}$$

The control voltage input is not used and is connected to a decoupling capacitor C_2 to prevent noise from affecting the trigger and threshold levels.

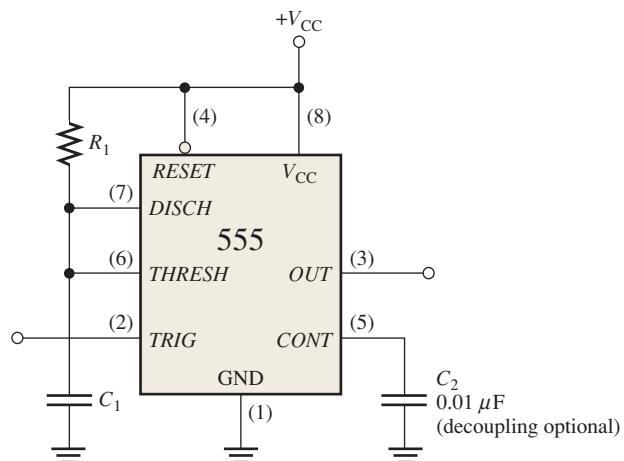


FIGURE 7–53 The 555 timer connected as a one-shot.

Before a trigger pulse is applied, the output is LOW and the discharge transistor Q_1 is *on*, keeping C_1 discharged as shown in Figure 7–54(a). When a negative-going trigger pulse is applied at t_0 , the output goes HIGH and the discharge transistor turns *off*, allowing capacitor C_1 to begin charging through R_1 as shown in part (b). When C_1 charges to $\frac{1}{3} V_{CC}$,

the output goes back LOW at t_1 and Q_1 turns *on* immediately, discharging C_1 as shown in part (c). As you can see, the charging rate of C_1 determines how long the output is HIGH.

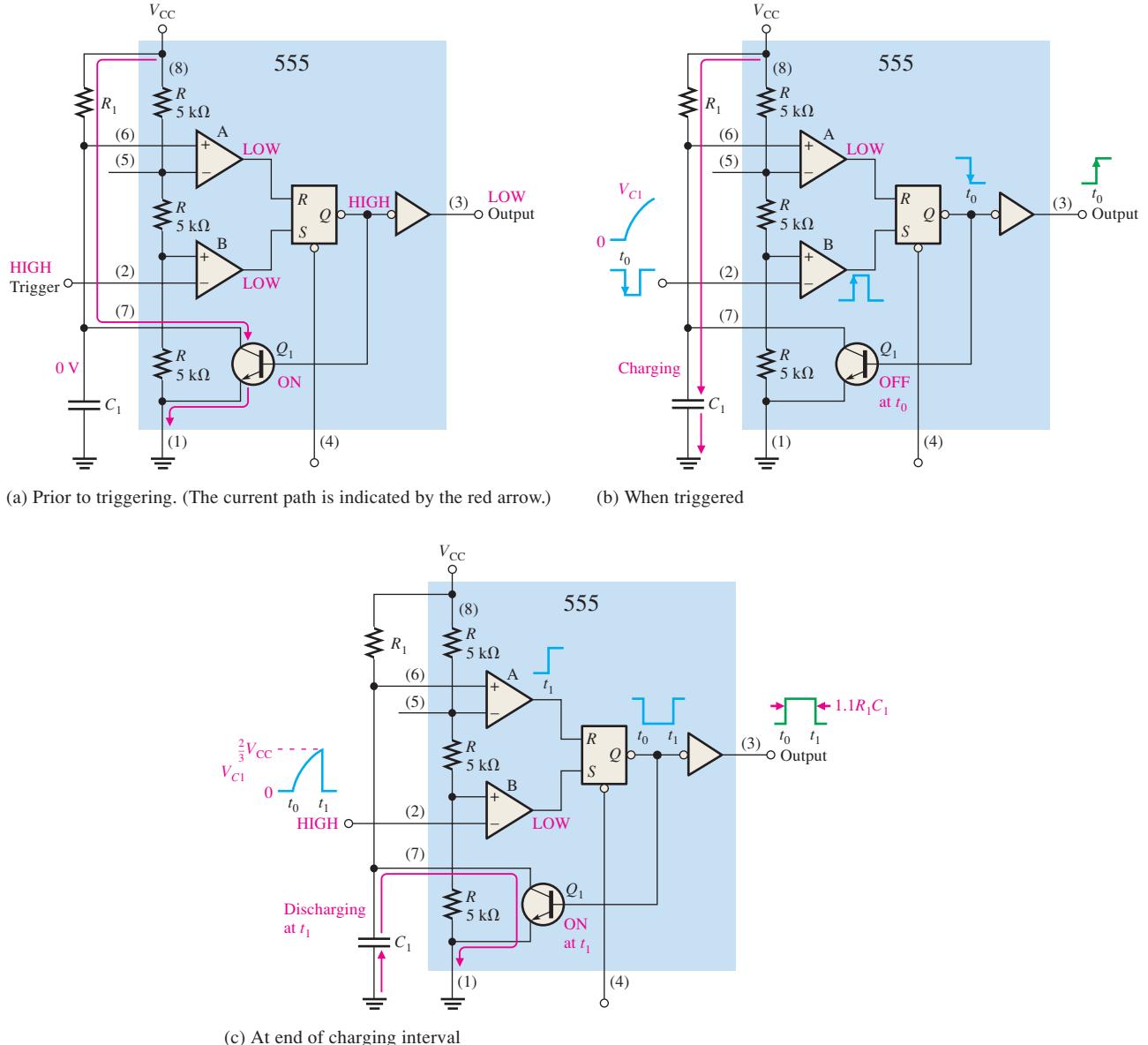


FIGURE 7-54 One-shot operation of the 555 timer.

EXAMPLE 7-13

What is the output pulse width for a 555 monostable circuit with $R_1 = 2.2 \text{ k}\Omega$ and $C_1 = 0.01 \mu\text{F}$?

Solution

From Equation 7-3 the pulse width is

$$t_W = 1.1R_1C_1 = 1.1(2.2 \text{ k}\Omega)(0.01 \mu\text{F}) = 24.2 \mu\text{s}$$

Related Problem

For $C_1 = 0.01 \mu\text{F}$, determine the value of R_1 for a pulse width of 1 ms.

One-Shot with VHDL

An example of a VHDL program code for a one-shot is as follows:



```

library ieee;
use ieee.std_logic_1164.all;

entity OneShot is
    port (Enable, Clk: in std_logic;
          Duration: in integer range 0 to 25;
          QOut: buffer std_logic);
end entity OneShot;

architecture OneShotBehavior of OneShot is
begin
    Counter: process (Enable, Clk, Duration)
        variable Flag      : boolean := true;
        variable Cnt       : integer range 0 to 25;
        variable SetCount : integer range 0 to 25;
    begin
        SetCount := Duration;
        if (Clk'EVENT and Clk = '1') then
            if Enable = '0' then
                Flag := true;
            end if;
            if Enable = '1' and Flag then
                Cnt := 1;
                Flag := false;
            end if;
            if Cnt = SetCount then
                Qout <= '0';
                Cnt := 0;
                Flag := false;
            else
                if Cnt > 0 then
                    Cnt := Cnt + 1;
                    Qout <= '1';
                end if;
            end if;
        end if;
    end process;
end architecture OneShotBehavior;

```



In normal operation, a one-shot produces only a single pulse, which can be difficult to measure on an oscilloscope because the pulse does not occur regularly. To obtain a stable display for test purposes, it is useful to trigger the one-shot from a pulse generator that is set to a longer period than the expected pulse width and trigger the oscilloscope from the same pulse. For very long pulses, either store the waveform using a digital storage oscilloscope or shorten the time constant by some known factor. For example, replace a $1000 \mu\text{F}$ capacitor with a $1 \mu\text{F}$ capacitor to shorten the time by a factor of 1000. A faster pulse is easier to see and measure with an oscilloscope.

SECTION 7–5 CHECKUP

1. Describe the difference between a nonretriggerable and a retriggerable one-shot.
2. How is the output pulse width set in most IC one-shots?
3. What is the pulse width of a 555 timer one-shot when $C = 1 \mu\text{F}$ and $R = 10 \text{ k}\Omega$?

7–6 The Astable Multivibrator

An **astable** multivibrator is a device that has no stable states; it changes back and forth (oscillates) between two unstable states without any external triggering. The resulting output is typically a square wave that is used as a clock signal in many types of sequential logic circuits. Astable multivibrators are also known as **pulse oscillators**.

After completing this section, you should be able to

- ◆ Describe the operation of a simple astable multivibrator using a Schmitt trigger circuit.
- ◆ Set up a 555 timer as an astable multivibrator.

Figure 7–55(a) shows a simple form of astable multivibrator using an inverter with hysteresis (Schmitt trigger) and an RC circuit connected in a feedback arrangement. When power is first applied, the capacitor has no charge; so the input to the Schmitt trigger inverter is LOW and the output is HIGH. The capacitor charges through R until the inverter input voltage reaches the upper trigger point (UTP), as shown in Figure 7–55(b). At this point, the inverter output goes LOW, causing the capacitor to discharge back through R , shown in part (b). When the inverter input voltage decreases to the lower trigger point (LTP), its output goes HIGH and the capacitor charges again. This charging/discharging cycle continues to repeat as long as power is applied to the circuit, and the resulting output is a pulse waveform, as indicated.

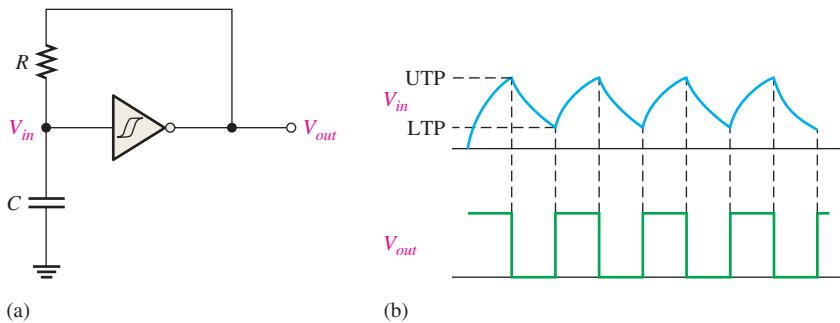


FIGURE 7–55 Basic astable multivibrator using a Schmitt trigger.

The 555 Timer as an Astable Multivibrator

A 555 timer connected to operate as an astable multivibrator is shown in Figure 7–56. Notice that the threshold input (*THRESH*) is now connected to the trigger input (*TRIG*). The external components R_1 , R_2 , and C_1 form the timing network that sets the frequency of oscillation. The $0.01 \mu\text{F}$ capacitor, C_2 , connected to the control (*CONT*) input is strictly for decoupling and has no effect on the operation; in some cases it can be left off.

InfoNote

Most systems require a timing source to provide accurate clock waveforms. The timing section controls all system timing and is responsible for the proper operation of the system hardware. The timing section usually consists of a crystal-controlled oscillator and counters for frequency division. Using a high-frequency oscillator divided down to a lower frequency provides for greater accuracy and frequency stability.

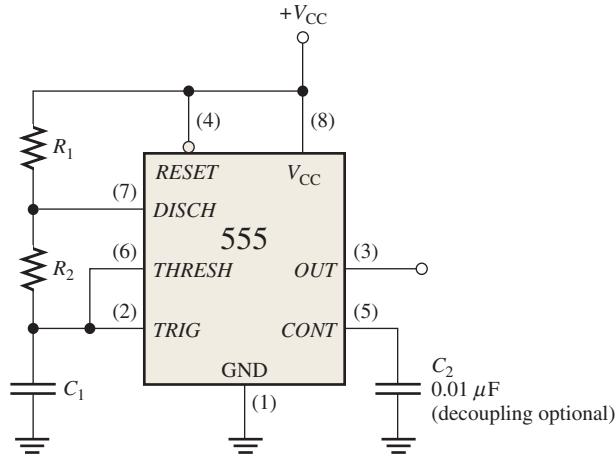


FIGURE 7–56 The 555 timer connected as an astable multivibrator (oscillator).

Initially, when the power is turned on, the capacitor (C_1) is uncharged and thus the trigger voltage (pin 2) is at 0 V. This causes the output of comparator B to be HIGH and the output of comparator A to be LOW, forcing the output of the latch, and thus the base of Q_1 , LOW and keeping the transistor off. Now, C_1 begins charging through R_1 and R_2 , as indicated in Figure 7–57. When the capacitor voltage reaches $\frac{1}{3} V_{CC}$, comparator B switches to its LOW output state; and when the capacitor voltage reaches $\frac{2}{3} V_{CC}$, comparator A switches to its HIGH output state. This resets the latch, causing the base of Q_1 to go HIGH and turning on the transistor. This sequence creates a discharge path for the capacitor through R_2 and the transistor, as indicated. The capacitor now begins to discharge, causing comparator A to go LOW. At the point where the capacitor discharges down to $\frac{1}{3} V_{CC}$, comparator B switches HIGH; this sets the latch, making the base of Q_1 LOW and turning off the transistor. Another charging cycle begins, and the entire process repeats. The

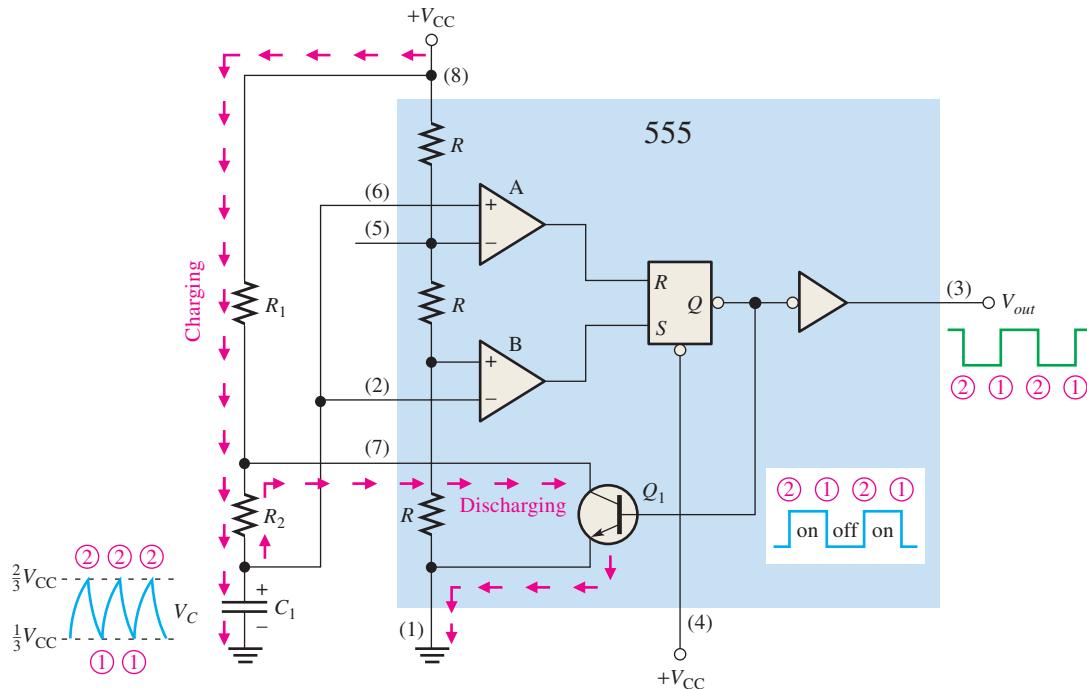


FIGURE 7–57 Operation of the 555 timer in the astable mode.

result is a rectangular wave output whose duty cycle depends on the values of R_1 and R_2 . The frequency of oscillation is given by the following formula, or it can be found using the graph in Figure 7–58.

$$f = \frac{1.44}{(R_1 + 2R_2)C_1} \quad \text{Equation 7-4}$$

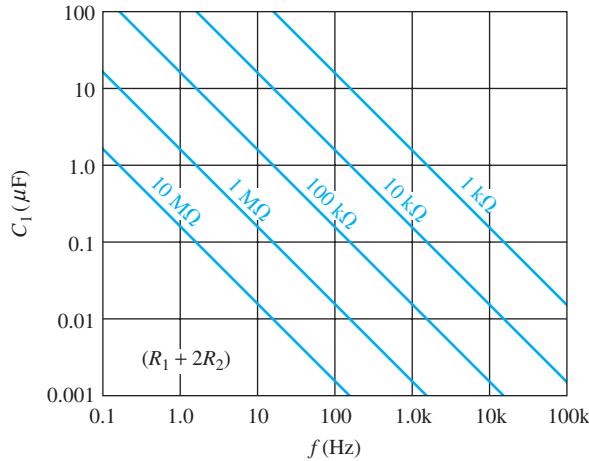


FIGURE 7-58 Frequency of oscillation as a function of C_1 and $R_1 + 2R_2$. The sloped lines are values of $R_1 + 2R_2$.

By selecting R_1 and R_2 , the duty cycle of the output can be adjusted. Since C_1 charges through $R_1 + R_2$ and discharges only through R_2 , duty cycles approaching a minimum of 50 percent can be achieved if $R_2 \gg R_1$ so that the charging and discharging times are approximately equal.

An expression for the duty cycle is developed as follows. The time that the output is HIGH (t_H) is how long it takes C_1 to charge from $\frac{1}{3} V_{CC}$ to $\frac{2}{3} V_{CC}$. It is expressed as

$$t_H = 0.7(R_1 + R_2)C_1 \quad \text{Equation 7-5}$$

The time that the output is LOW (t_L) is how long it takes C_1 to discharge from $\frac{1}{3} V_{CC}$ to $\frac{2}{3} V_{CC}$. It is expressed as

$$t_L = 0.7R_2C_1 \quad \text{Equation 7-6}$$

The period, T , of the output waveform is the sum of t_H and t_L . This is the reciprocal of f in Equation 7–4.

$$T = t_H + t_L = 0.7(R_1 + 2R_2)C_1$$

Finally, the duty cycle is

$$\begin{aligned} \text{Duty cycle} &= \frac{t_H}{T} = \frac{t_H}{t_H + t_L} \\ \text{Duty cycle} &= \left(\frac{R_1 + R_2}{R_1 + 2R_2} \right) 100\% \end{aligned} \quad \text{Equation 7-7}$$

To achieve duty cycles of less than 50 percent, the circuit in Figure 7–56 can be modified so that C_1 charges through only R_1 and discharges through R_2 . This is achieved with a diode, D_1 , placed as shown in Figure 7–59. The duty cycle can be made less than 50 percent by making R_1 less than R_2 . Under this condition, the expression for the duty cycle is

$$\text{Duty cycle} = \left(\frac{R_1}{R_1 + R_2} \right) 100\% \quad \text{Equation 7-8}$$

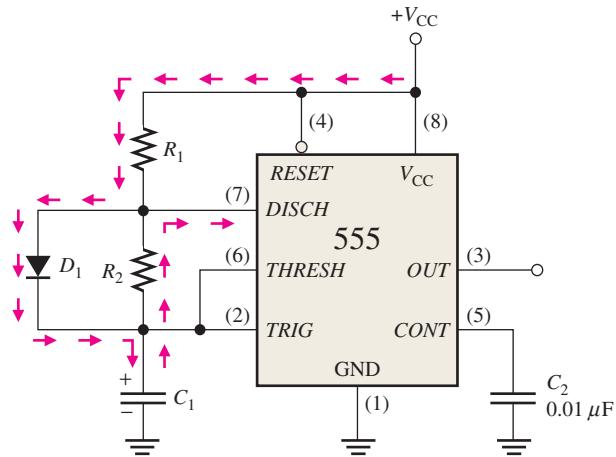


FIGURE 7-59 The addition of diode D_1 allows the duty cycle of the output to be adjusted to less than 50 percent by making $R_1 < R_2$.

EXAMPLE 7-14

A 555 timer configured to run in the astable mode (pulse oscillator) is shown in Figure 7-60. Determine the frequency of the output and the duty cycle.

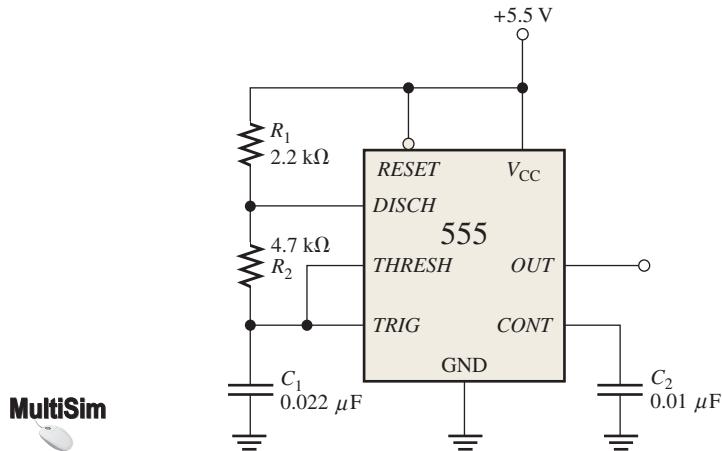


FIGURE 7-60 Open file F07-60 to verify operation.

Solution

Use Equations 7-4 and 7-7.

$$f = \frac{1.44}{(R_1 + 2R_2)C_1} = \frac{1.44}{(2.2 \text{ k}\Omega + 9.4 \text{ k}\Omega)0.022 \mu\text{F}} = 5.64 \text{ kHz}$$

$$\text{Duty cycle} = \left(\frac{R_1 + R_2}{R_1 + 2R_2} \right) 100\% = \left(\frac{2.2 \text{ k}\Omega + 4.7 \text{ k}\Omega}{2.2 \text{ k}\Omega + 9.4 \text{ k}\Omega} \right) 100\% = 59.5\%$$

Related Problem

Determine the duty cycle in Figure 7-60 if a diode is connected across R_2 as indicated in Figure 7-59.