

Lecture-14

LATCHES: The latch is a type of bintable storage DEVICE

The S-R Latch:

 


Fig: Active High input S-R Latch

 


Fig: Logic symbol for Active-High input S-R Latch

Truth table for active-High input S-R Latch

Inputs		Outputs		Comments
S	R	Q	\bar{Q}	
0	0	NC	NC	No change Latch
0	1	0	1	Latch Reset
1	0	1	0	Latch Set
1	1	0	0	Invalid condition

we will never operate latch in this condition

 


Fig: Active-LOW input
S-R latch

 


Fig: Logic symbol of
S-R latch

Input		Output		Comments
\bar{S}	\bar{R}	Q	\bar{Q}	
0	0	1	1	Invalid condition
0	1	1	0	Latch Set
1	0	0	1	Latch Reset
1	1	NC	NC	No change, Latch

we will never
operate latch
in this condition

A Gated SR Latch:

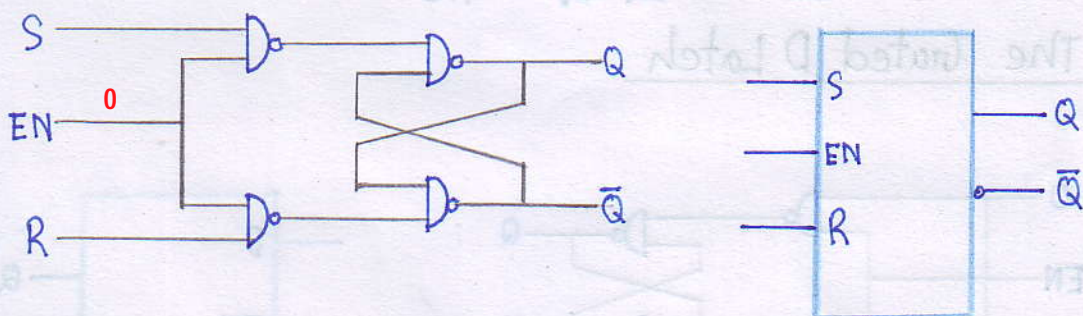



Fig: Logic diagram

Truth table for gated SR Latch

EN	S	R	Q	\bar{Q}	Comments
0	X	X	NC	NC	No change. Latch remains in previous state
1	0	0	<u>NC</u>	<u>NC</u>	
1	0	1	0	1	Latch Reset
1	1	0	1	0	Latch Set
1	1	1	1	1	Invalid condition

(Device is not operated in this condition)

 Determine Q if the gated S-R Latch is initially RESET.



The Gated D Latch

 


Fig: Logic diagram


 


Fig: Logic symbol

Truth table for D Latch

Inputs		Outputs		Comments
EN	D	Q	\bar{Q}	
0	X	Nc	Nc	No Change
1	1	1	0	SET
1	0	0	1	RESET

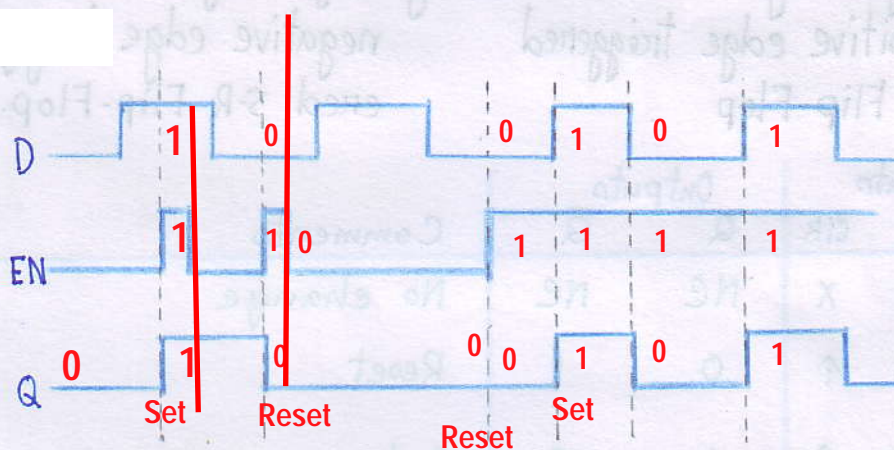

The gated latches control the flow of information from the input to the output, based upon the level of the enable pin (EN). If the EN=0, the output of the device does not change. If EN=1, the output changes based upon the values from truth table.

Determine Q if the D-Latch is initially Reset.

EDGE-TRIGGERED FLIP-FLOPS

A flip-flops is a synchronous bistable. An edge-triggered flip-flops changes state either at the positive edge (rising edge) or at the negative edge (falling edge) of the clock pulse and is sensitive to its inputs only at this transition of the clock.

The Edge-Triggered S-R Flip-Flops:

 


Fig: Logic symbol of positive edge triggered S-R Flip-Flop


 


Fig: Logic symbol of negative edge triggered S-R Flip-Flop.

Inputs			Outputs		Comments
S	R	clk	Q	\bar{Q}	
0	0	X	NC	NC	No change
0	1	↑	0	1	Reset
1	0	↑	1	0	Set
1	1	↑	?	?	Invalid

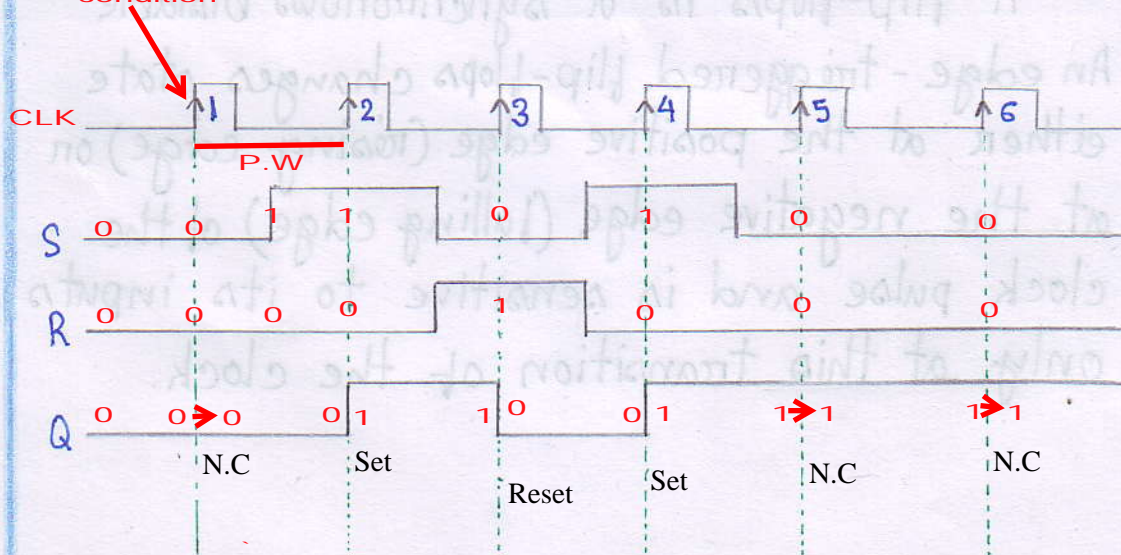The rising edge of the clock is when the clock signal is going from low to high condition



Positive edge triggered

Determine Q if the n Flip-Flop is initially at Reset state

A method of Edge-Triggering


 


Fig: Pulse transition detector

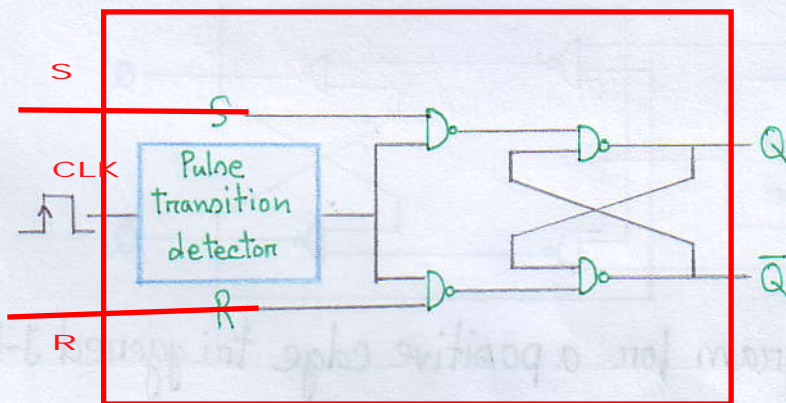

S-R Flip-Flop

The job of the pulse transition detector is to convert the level sensitivity of the EN pin of a gated S-R latch to edge sensitivity and convert the system to a S-R Flip-flop